

# Topic 6

## Latches and Flip Flops

# Introduction


- Combinational Circuit
  - A digital circuit whose output depends only upon the ***present combination*** of its inputs
- Sequential Circuit
  - A digital circuit whose output depends ***not only*** upon the ***present input*** values, ***but also the history*** of input and output values
- Beginning from this lecture, we will:
  - Learn sequential circuits
  - Design a new type of building blocks, **latch & flip-flop**, that store value of a bit, a sequential circuit
  - Combine the blocks to build multi-bit storage – a **register**

# Recall: Timing Diagrams for Gates

xy	F
0 0	0
0 1	0
1 0	0
1 1	1



x+y	F
0 0	0
0 1	1
1 0	1
1 1	1

x	F
0	1
1	0

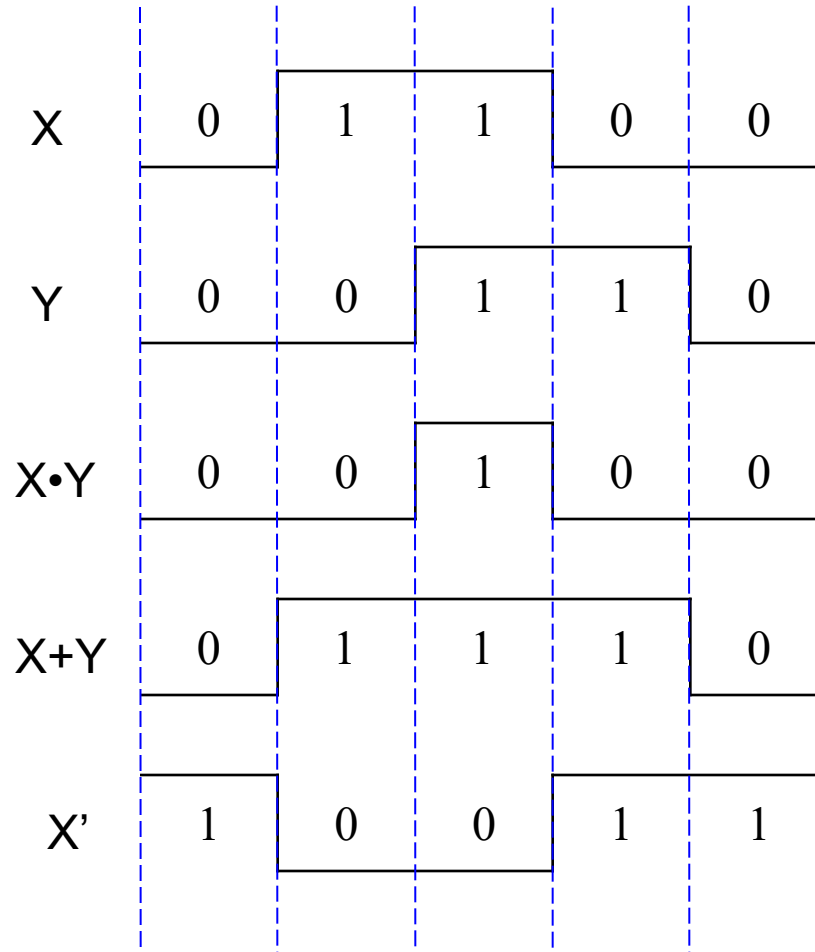

# Reality of Combinational Circuit


## Non-Ideal Gate Behavior -- Delay

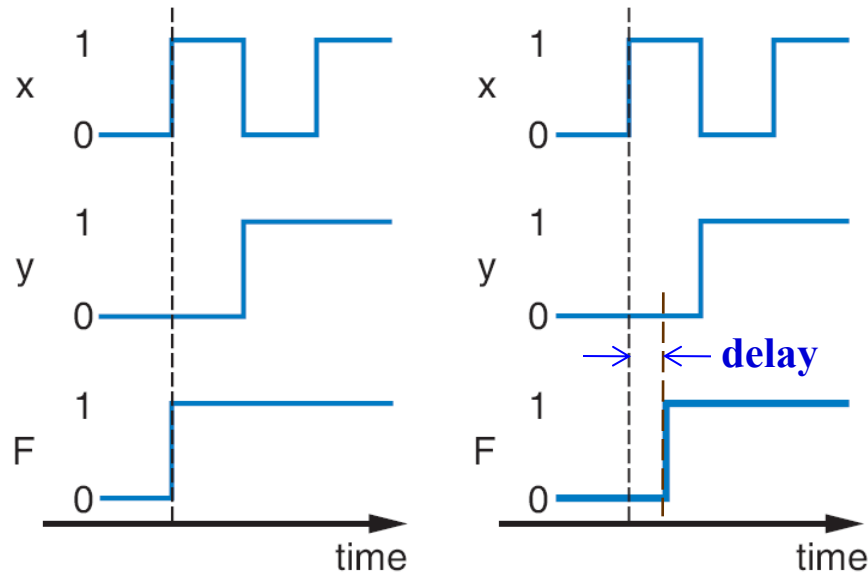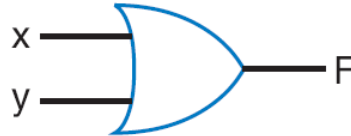

- Real gates have some delay
  - Outputs don't change immediately after inputs change

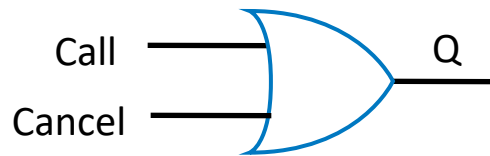
# Example of Needing Bit Storage

- Flight attendant call button
  - Button pressed: provides a “1”
  - Press call: light turns on
    - **Stays on** after button released (
  - Press cancel: light turns off
    - **Stays off** after the button is released
  - Circuit needs to “memorize” the input
  - Combinational circuit doesn’t work




Q=1 when Call=1, but doesn't stay 1 when Call returns to 0

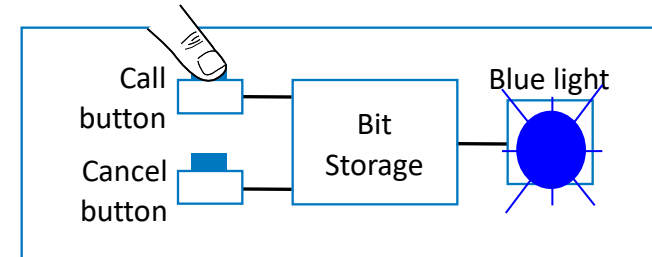
*Need some form of “memory” in the circuit*



1. Call button pressed – light turns on

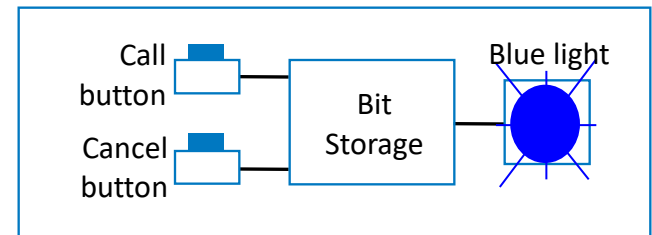


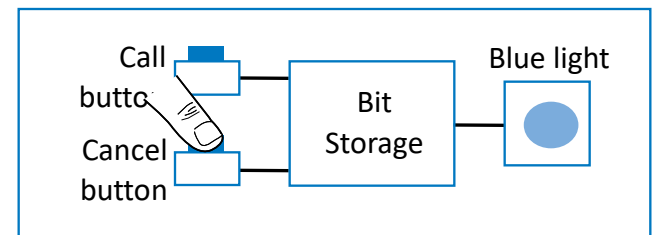
2. Call button released – light **stays on**



3. Cancel button pressed – light turns off

 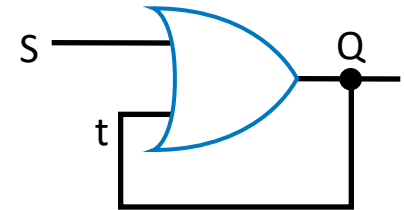
# First Attempt at Implementation of Bit Storage

- We send output back to input to memorize it
  - Does circuit on the right do what we want?
    - Once Q becomes 1 (when S=1), Q stays in 1
    - But forever – no value of S can bring Q back to 0


 
# Concepts of Sequential Circuit

- Sequential circuit
  - Combinational circuit with feedbacks










- Due to the feedback, output of a sequential circuit is decided by
    - Present inputs, and
    - Past input sequence and
    - Past outputs sequence
- Timing concepts
  - input-output propagation delay
  - clock
  - Other timing issues

# Second Attempt at Bit Storage – SR Latch

- Cross-coupled NOR gates
  - S: set (or preset) to 1
  - R: reset (or clear) to 0



Recall...

     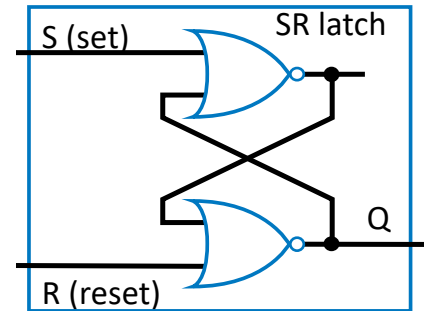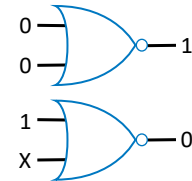



  
# Example Using SR Latch for Bit Storage

- SR latch can serve as a **bit storage**, for example:
  - Call=1 : sets Q to 1
    - Q stays 1 even after Call=0
  - Cancel=1 : resets Q to 0
- But, there's a problem...




# Problem with SR Latch

 - Problem
  - If  $S=1$  and  $R=1$ , we don't know what value  $Q$  will take when they both return to 0 *simultaneously*



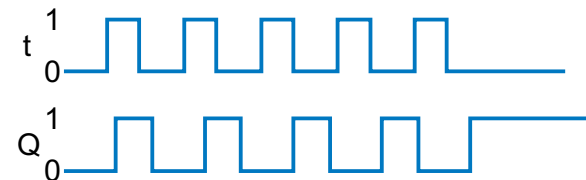$Q$  may oscillate. Then, because one path will be slightly longer than the other,  $Q$  will eventually settle to 1 or 0 – but we don't know which.



# Representation of SR Latch

- When discussing latches and flip-flops, we use
  - **present state** to represent current value of the Q output
  - **next state** to represent the new value of Q output responding to the current inputs and feedback of current output
- Characteristic table

S(t)	R(t)	Q(t)	Q(t+Δ) → Q <sup>+</sup>	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	



		Q <sup>+</sup>	
		S(t)	R(t)
R(t) Q(t)	0	0	1
	1	0	1
	1	1	X
	1	0	X

- Characteristic equation

$$Q^+ = S + R'Q$$
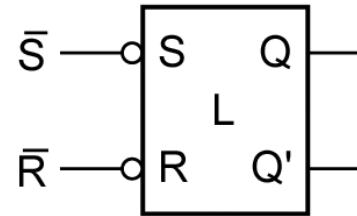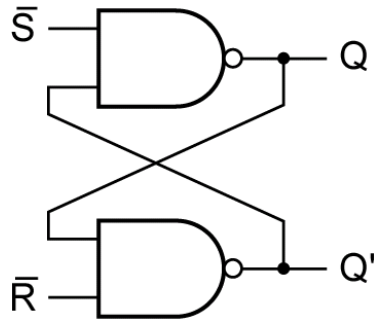
# Alternative Implementation of SR Latch

- The cross-coupled SR latch can be implemented using NAND gates




- Characteristic table

S	R	Q	Q <sup>+</sup>	
0	0	0	X	not allowed
0	0	1	X	
0	1	0	1	set
0	1	1	1	
1	0	0	0	reset
1	0	1	0	
1	1	0	0	hold
1	1	1	1	

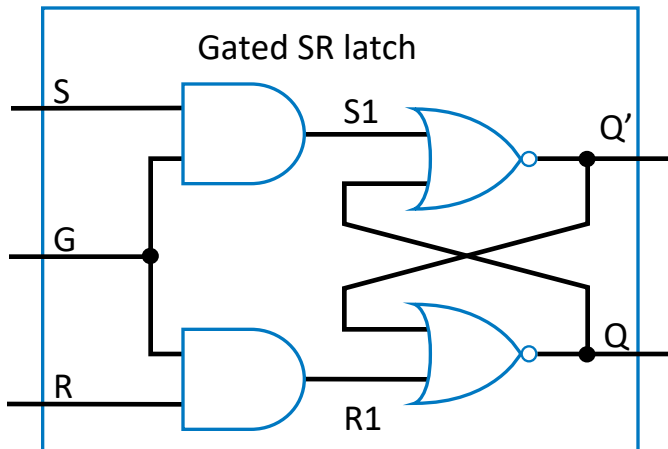
# Gated SR Latch

- SR latch is enabled by a gate control signal G



Characteristic Table

G	S	R	Q <sup>+</sup>
0	x	x	Q; Latch locked
1	0	0	Q; Hold state
1	0	1	0; Reset state
1	1	0	1; Set state
1	1	1	not allowed

 


Gated SR latch  
symbol

# Solution to SR Latch Restriction
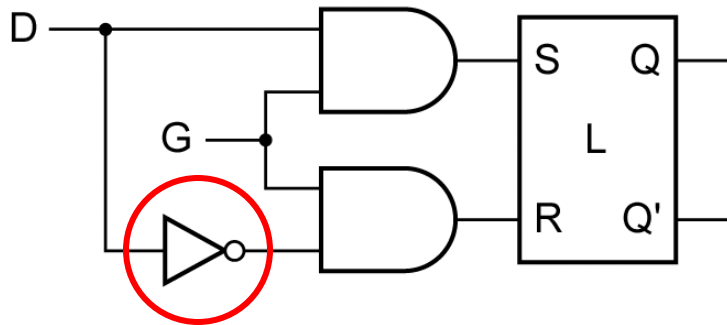
## – Gated D Latch


- Solution to the unstable state problem caused by  $S = R = 1$  in SR latch



Characteristic Table

G	D	Q <sup>+</sup>
1	0	0
1	1	1
0	X	Q


 
- The input value is stored into the latch only when gate control G has high level – **Level Sensitive**



D latch  
symbol

  
# Gated D Latch – Transparent Latch

- Properties of the D latch
  - D latch is used as a **temporary storage** for a bit
  - The binary information at the data input of the D latch is **copied** to the Q output when the control input G is high (or enabled)
  - The output Q follows changes on the data input D as long as the control input G is enabled, so called a **transparent** latch


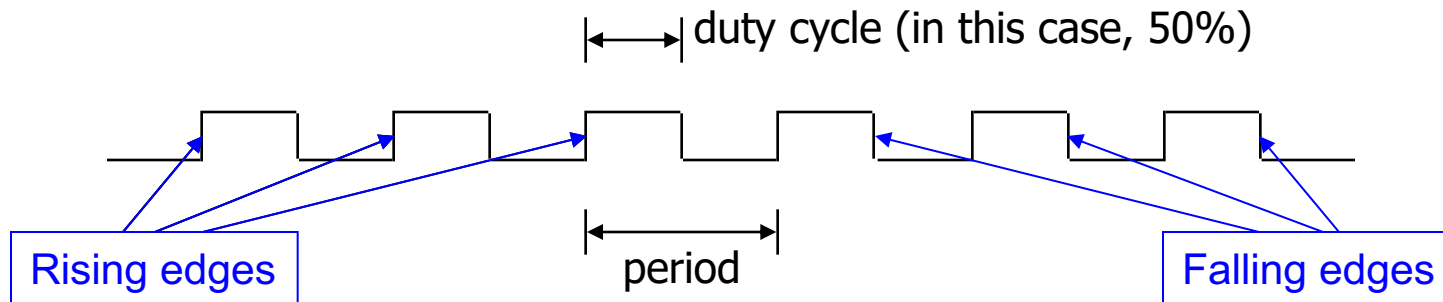
# A Typical Control Input – Clock Signal

- Periodic pulse train used in sequential circuit to synchronize circuit behaviors




- ***Clock period***: time interval between pulses
- ***Clock cycle***: one such time interval
- ***Clock frequency***:  $1/\text{period}$

Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns



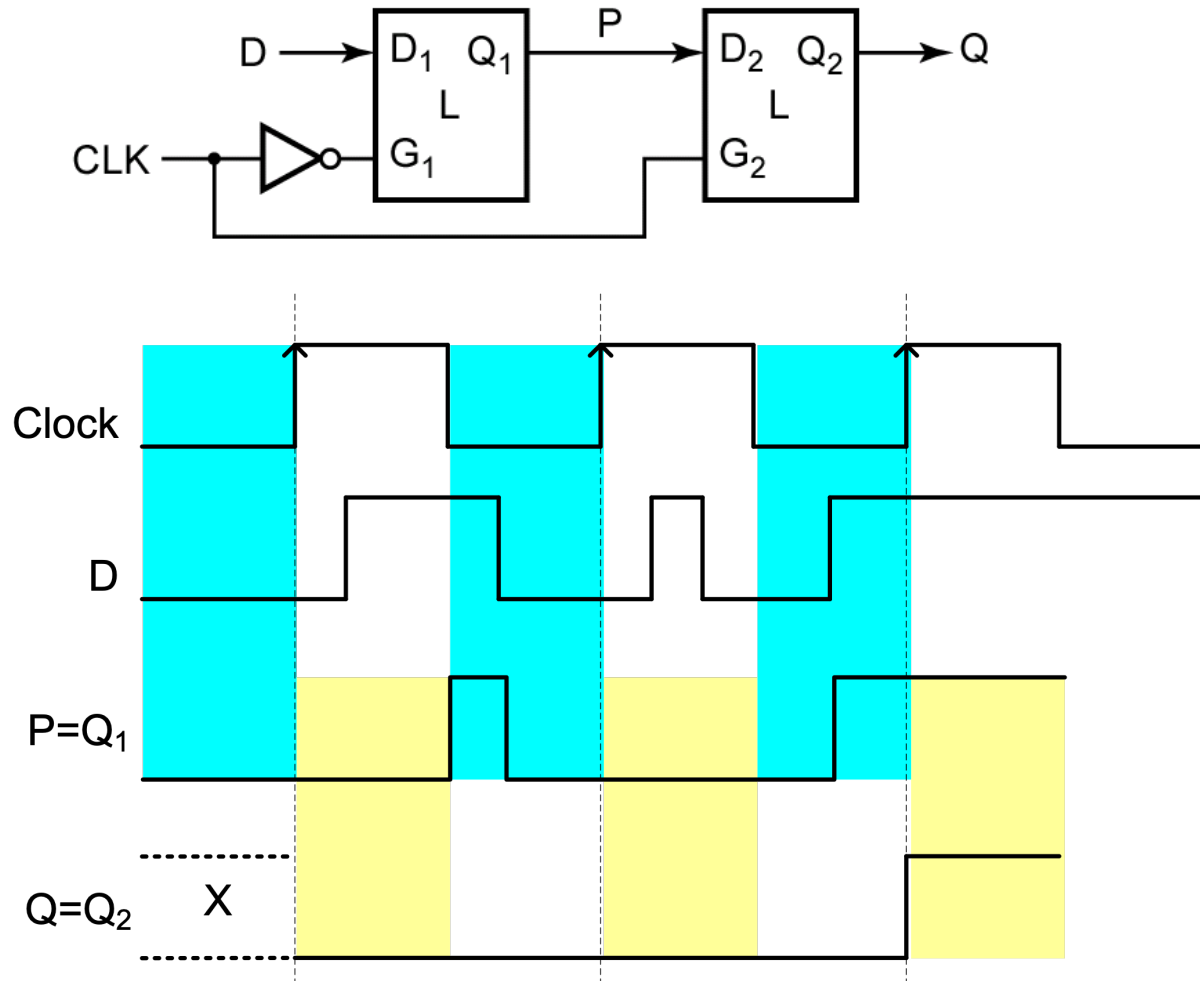
# Rising-Edge Triggered D Flip Flop


- Rising-edge triggered Master-Slave D flip flop


 
# Gate-level Implementation of Rising-Edge Triggered D Flip Flop



Alternative Implementation

 


clock	D	Q <sup>+</sup>
$\uparrow$	0	0
$\uparrow$	1	1
0	X	Q
1	X	Q


Characteristic equation:  
 $Q^+ = D$  (at active clock edges)
 
# Rising-Edge Triggered D Flip Flop


- Properties of the rising edge triggered D Flip Flop
  - The output changes only at the rising edges of the clock signal – **Edge Sensitive**
  - The output Q gets the value of input D at the time point of rising edge of clock





# Symbols for D Flip-Flop

 

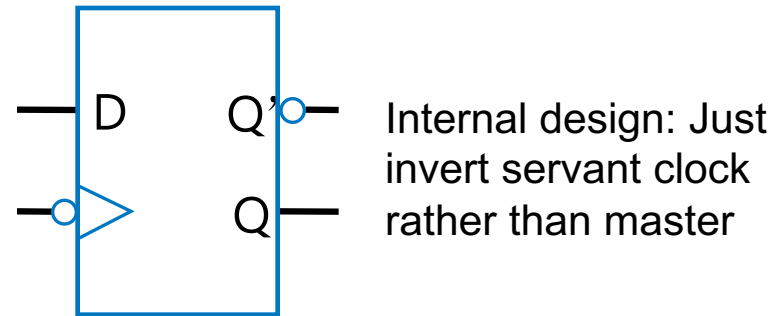Symbol for rising-edge triggered D flip-flop




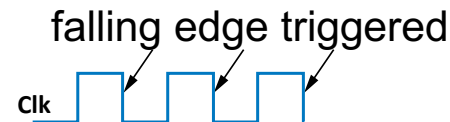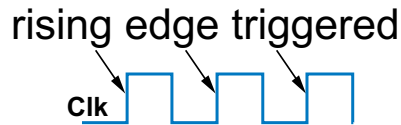Symbol for falling-edge triggered D flip-flop


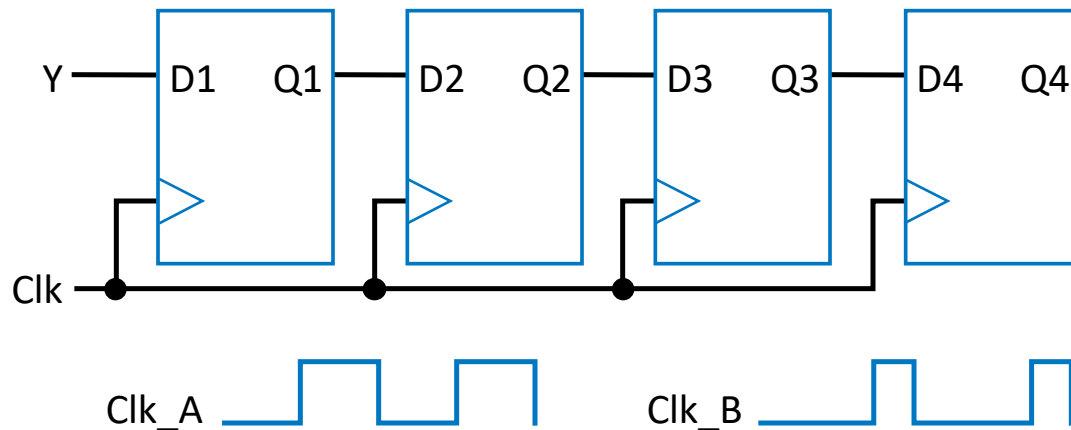
# Application of D Flip-Flop



- Solves problem of concatenated D latches when  $G=1$ 
  - In figure below, signal travels through exactly one flip-flop, for either Clk\_A or Clk\_B
  - On each rising edge of Clk, all four flip-flops are loaded simultaneously, doesn't matter how long Clk is 1.



# Flip Flop vs. Latch

- **Both are storage elements in sequential circuits**
- **Flip flop**
  - **edge-sensitive**, the input matters only at active edges (rising or falling)
  - behaviors are **synchronous** to the clock signal
- **Latch**
  - **level-sensitive**, the input matters whenever control has active level (high or low)
  - behaviors are **asynchronous** to the clock signal

# Flip Flop vs. Latch

  

# Flight-Attendant Call Button Using D Flip-Flop


- D flip-flop will store bit
- Inputs are Call, Cancel, and present output Q of D flip-flop
- Truth table

Call	Cancel	Q	$Q^+ = D$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1





		Cancel Q			
		00	01	11	10
Call	0	0	1		0
	1	1	1	1	1
 
$$Q^+ = D = \text{Call} + \text{Cancel}' Q$$






# Rising Edge-triggered J-K Flip Flop

  


J	K	Q <sup>+</sup>
0	0	Q
0	1	0
1	0	1
1	1	Q'

Characteristic equation:  
 $Q^+ = JQ' + K'Q$


# Rising Edge-triggered T Flip Flop

 

Implemented with D ff

 


Implemented with JK ff

 



clock	T	Q <sup>+</sup>
	0	Q
	1	Q'

 Characteristic equation:  
 $Q^+ = T'Q + TQ' = T \oplus Q$



  
# Basic Register

- Typically, we store multi-bit items
  - e.g., storing a 4-bit binary number
- **Register**: multiple flip-flops sharing clock signal




 
# Example Using Registers: Temperature Display

- Temperature history display
  - Sensor outputs temperature as 5-bit binary number
  - Timer pulses C every hour
  - Record temperature on each pulse, display last three recorded values




# Example Using Registers: Temperature Display

- Use three 5-bit registers

 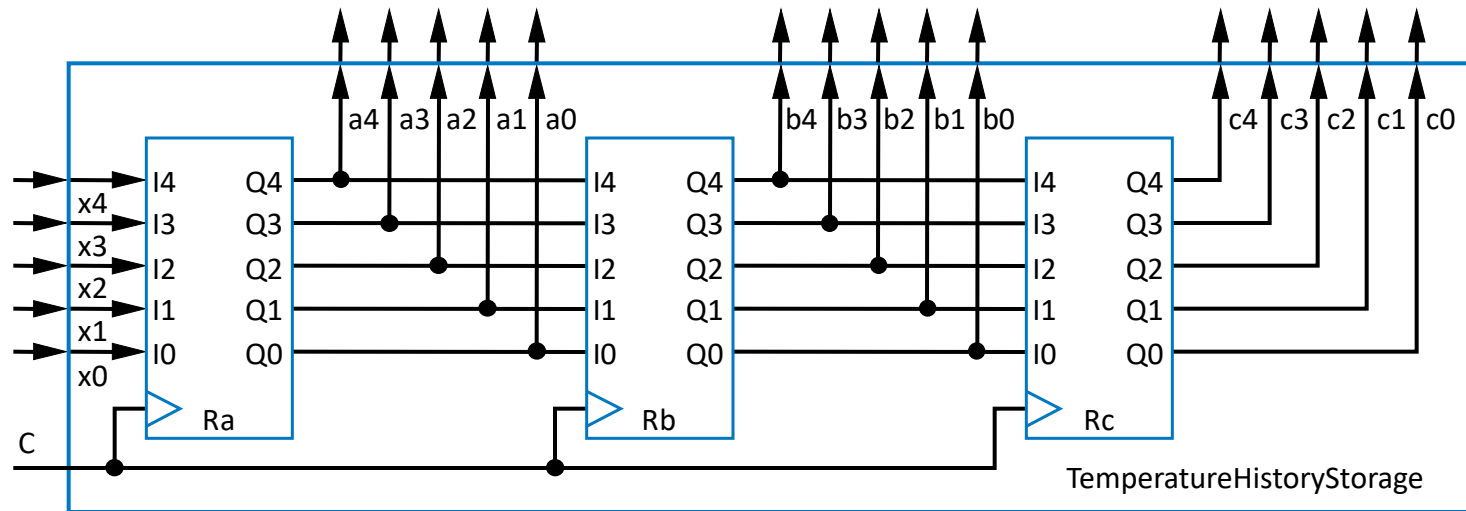


# Big Picture – Simplified CPU

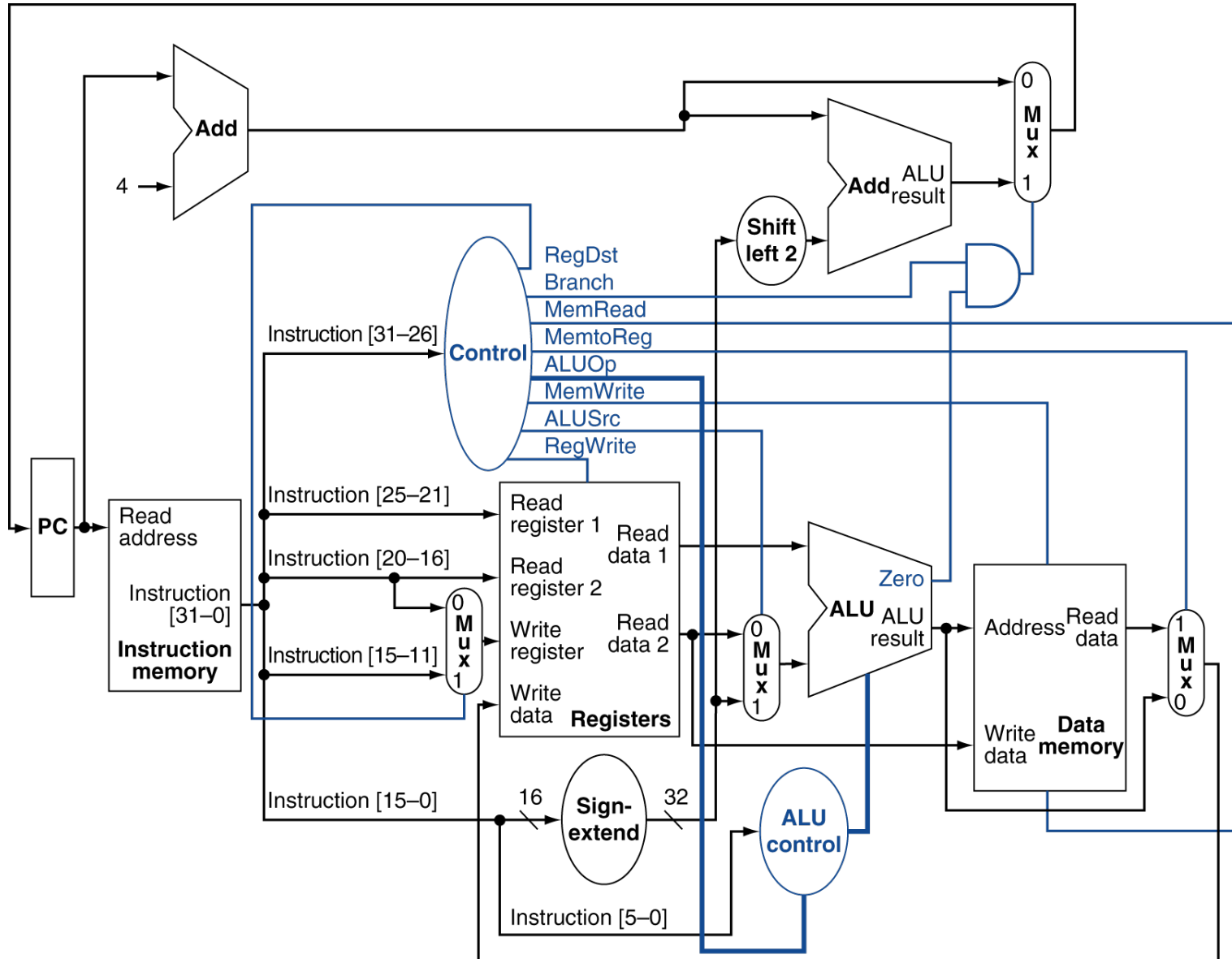

 
# Implementation of Asynchronous Control Input

Control signals decides the output value directly independent of the clock signal


 
# Control Inputs for Flip Flops


- Asynchronous:
  - control signals do not depend on the clock signal
- Synchronous:
  - control signals depend on the clock signal
- Active low:
  - It controls when it's low
- Active high:
  - It controls when it's high





 
# Asynchronous Control Input

- D flip flop with active low asynchronous Clear



 
# Implementation of Synchronous Control Input

- Synchronous Clear
  - control signal depends on the active edge (either rising or falling) of the clock signal




 
# Flip-Flops with Control Inputs

- D flip flop with active low synchronous Clear


 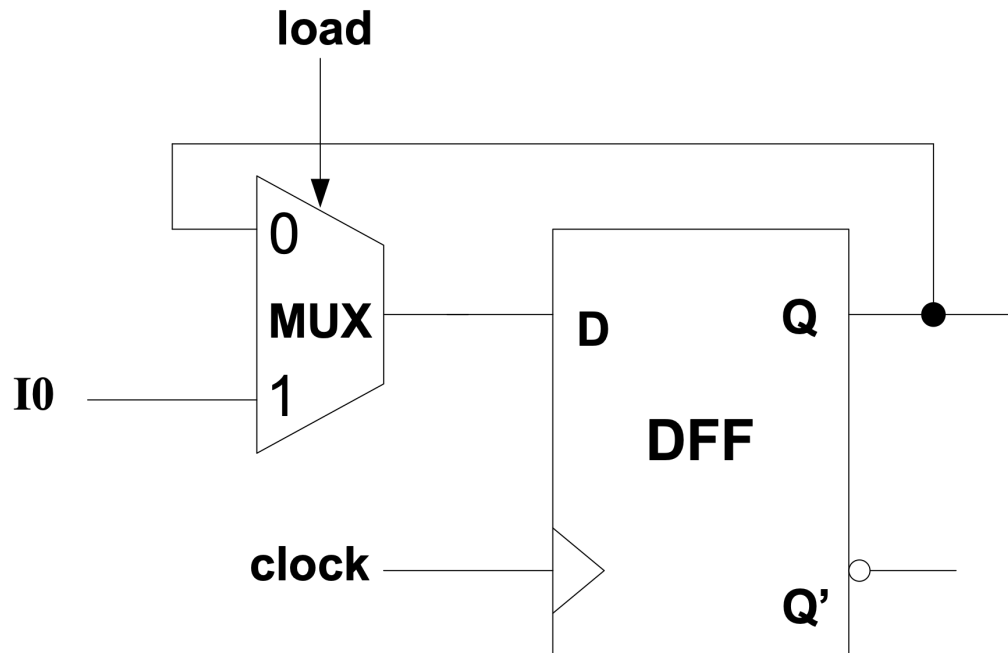
# Register with Synchronous Parallel Load

- Add 2x1 mux to each flip-flop
- Register's load input selects mux input to pass
  - Either existing flip-flop value, or new value to load



One bit of the register with  
synchronous active high Load

# Register with Synchronous Parallel Load

- D flip flop with active low synchronous Clear

