

# **ECE2150J Intro to Circuits**

## **Chapter 4. Circuit Theorems**

Instructor: Dr. Yuljae Cho, Global College

## 4.1 Introduction

- **A major advantage** of analyzing circuits using skills in Chapter 2 and 3 is that we can analyze a circuit without tampering with its original configuration. **A major disadvantage** of this approach is that for a large, complex circuit, tedious computation is involved.
- Therefore, it is useful if we can **simplify circuits**. In this chapter, we will study some theorems, such as, **Thevenin and Norton** (for linear circuit).

## 4.2 Linearity

- A linear circuit is one whose output/response is **linearly** related to its input/excitation.
- **The linearity property** is a combination of both the **homogeneity (scaling)** property and the **additivity** property.
- **A circuit is linear if it is both additive and homogeneous.**

- **Homogeneity** requires that if the input is multiplied by a constant, then the output is multiplied by the same constant.
- e.g. If  $y = ax$ , then  $a \cdot (kx) = ky$   
because  $a \cdot (\textcolor{red}{k}x) = k(ax)$
- In a circuit, homogeneity can be seen, for example, in Ohm's law.
- $V = iR$ , and if the current increased by a constant  $k$ , then  **$ki \cdot R = k \cdot V$**

- Inhomogeneity example

$y = ax^2$ , then  $a(kx)^2 = k^2y$ , because  $ak^2x^2 = k^2(ax^2)$

The output is **NOT** multiplied by the same constant.

In a circuit, the relationship between **power** and **voltage/current is nonlinear**,  $P = i^2R = V^2/R$ .

- **Additivity** property requires that the response to a sum of inputs is the sum of the responses to each input applied separately.
- Assuming input  $x_1$  produces output  $y_1$ ; input  $x_2$  produces output  $y_2$  ( $y_1 = ax_1$ ,  $y_2 = ax_2$ )
- e.g.  $y = ax$  where input  $x = x_1 + x_2$   
 $\rightarrow a(x_1 + x_2) = ax_1 + ax_2 = y_1 + y_2$
- A function with a square law, e.g.  $y = ax^2$ , does not show additivity.

**Example 4.1** For the circuit in Fig. 4.2, find  $I_o$  when  $v_s = 12$  V and  $v_s = 24$  V. This example illustrates the homogeneity property.

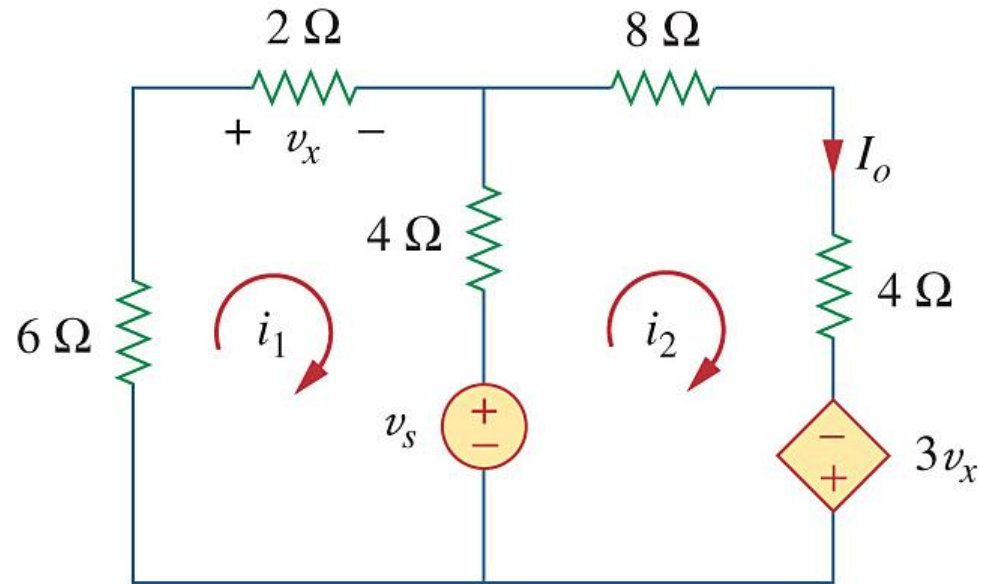


Figure 4.2

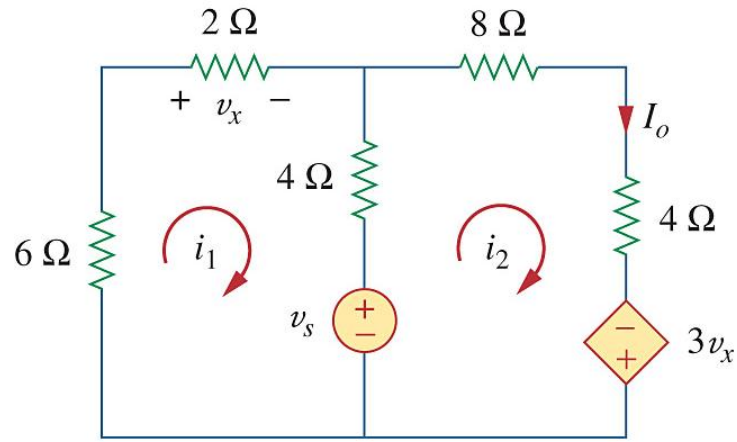


Figure 4.2

By using the inspection method

$$\begin{bmatrix} 6 + 2 + 4 & -4 \\ -4 & 4 + 8 + 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_s \\ 3v_x + v_s \end{bmatrix}$$

Because  $V_x = 2i_1$

$$\begin{bmatrix} 6 + 2 + 4 & -4 \\ -4 & 4 + 8 + 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_s \\ 6i_1 + v_s \end{bmatrix}$$

$$\begin{bmatrix} 6 + 2 + 4 & -4 \\ -4 - 6 & 4 + 8 + 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_s \\ v_s \end{bmatrix}$$



$$\begin{bmatrix} 12 & -4 \\ -10 & 16 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_s \\ v_s \end{bmatrix}$$

$I_o = i_2$  and thus get a solution for  $i_2$  using Cramer's rule

$$\Delta = \begin{vmatrix} 12 & -4 \\ -10 & 16 \end{vmatrix} = 152 \quad \Delta_2 = \begin{vmatrix} 12 & -v_s \\ -10 & v_s \end{vmatrix} = 2v_s \quad I_o = i_2 = \frac{\Delta_2}{\Delta} = \frac{v_s}{76}$$

When  $v_s = 12$  V,

$$I_o = \frac{12}{76} = \frac{3}{19} \text{ (A)}$$

When  $v_s = 24$  V,

$$I_o = \frac{24}{76} = \frac{6}{19} \text{ (A)}$$

### Homogeneous circuit

- $V_s \rightarrow I_o$
- $2V_s \rightarrow 2I_o$

## 4.3 Superposition

- Superposition principle is based on **additivity**.
- A linear circuit with **more than one independent source**: the total response is the sum of the individual responses.
- Calculate the contribution of each independent source **separately** and **add all the contributions** to find the total contribution.

- To apply the superposition principle, we must keep three points in mind:
  - (1) Only one independent source at a time.** All other independent sources are **turned off**
    - Voltage source: a short circuit (0 V)
    - Current source: an open circuit (0 A)
  - (2) Dependent sources are left intact** because they are controlled by circuit variables.
  - (3) Superposition is based on linearity:** Not applicable to Power

# Linear circuit: homogeneous + additive

- Linear circuit

$$x_1 \rightarrow y_1; x_2 \rightarrow y_2$$

$$\text{then, } ax_1 + bx_2 \rightarrow ay_1 + by_2$$

- Superposition

(1) contribution from input  $x_1$ :  $ax_1 \rightarrow ay_1$

(2) contribution from input  $x_2$ :  $bx_2 \rightarrow by_2$

adding all the contributions:  $ay_1 + by_2$

## Example 4.3



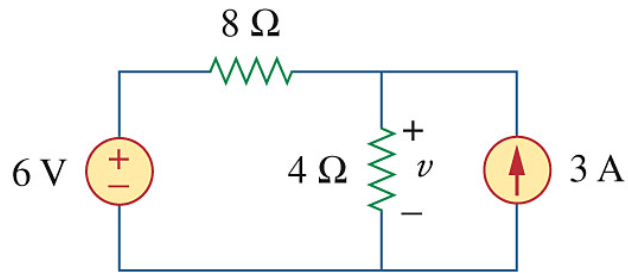


Figure 4.6

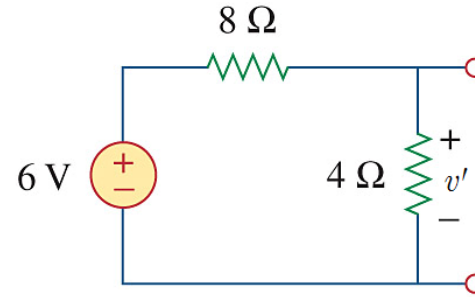

(a)

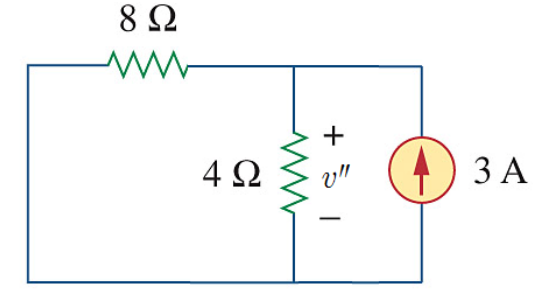

(b)

Figure 4.7

By superposition, output  $v = v' + v''$  where  $v'$  and  $v''$  are the contributions by the voltage and current source, respectively.

$$v' = \frac{4}{8+4} \times 6 = 2 \text{ (V)}$$

$$v'' = 3 \times (4 \parallel 8) = 3 \times \frac{4 \times 8}{4+8} = 8 \text{ (V)}$$

$$v = v' + v'' = 2 + 8 = 10 \text{ [V]}$$

**Practice Problem 4.4** Use superposition to find  $v_x$  in the circuit of Fig. 4.11.


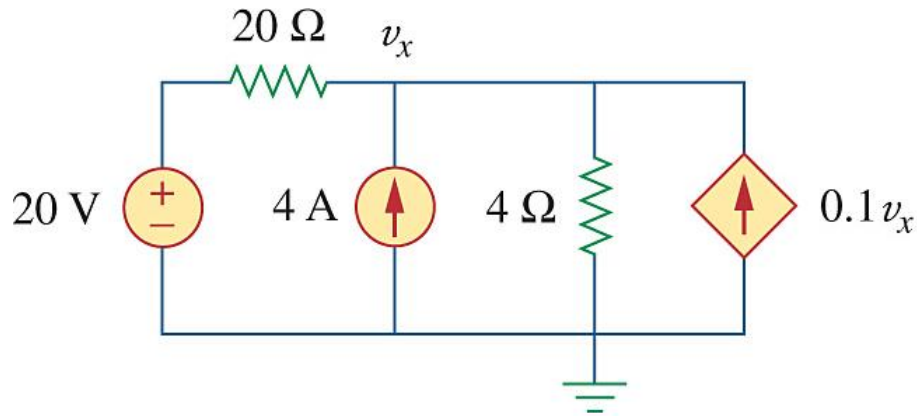


Figure 4.11

Voltage source: a short circuit (0 V)

Current source: an open circuit (0 A)
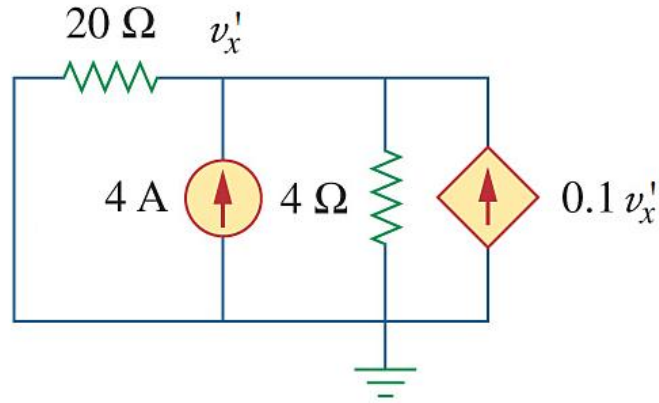
### (i) Contribution from the current source




$$\text{Let } v_x = v'_x + v''_x$$

Set the voltage source to zero,

$$\frac{v'_x}{20} - 4 + \frac{v'_x}{4} - 0.1v'_x = 0 \Rightarrow v'_x = 20 \text{ (V)}$$
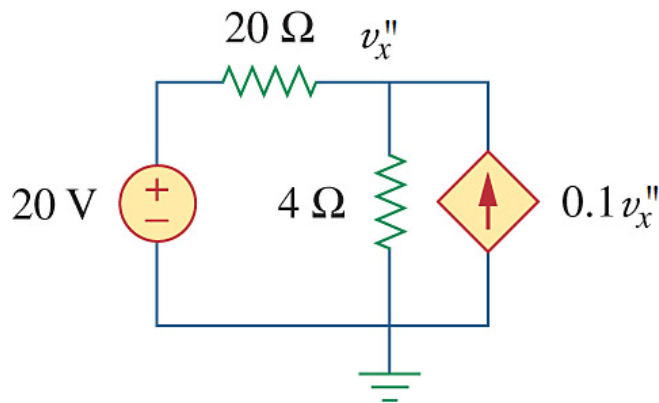
### (ii) Contribution from the potential source




Set the current source to zero,

$$\frac{v''_x - 20}{20} + \frac{v''_x}{4} = 0.1v''_x \Rightarrow v''_x = 5 \text{ (V)}$$

$$v_x = v'_x + v''_x = 25 \text{ (V)}$$

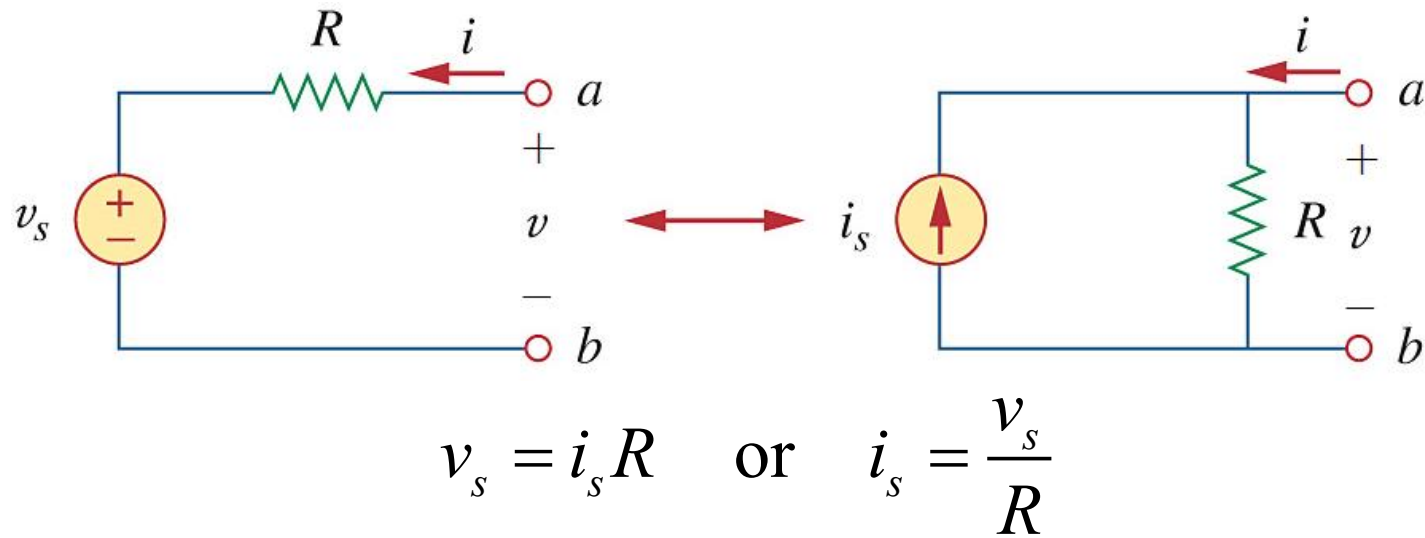
## 4.4 Source Transformation

- A source transformation is a tool for **simplifying circuits**.
- The source transformation is the process of replacing a **voltage source in series with a resistor** by a **current source in parallel with a resistor**, or vice versa.





## Proof

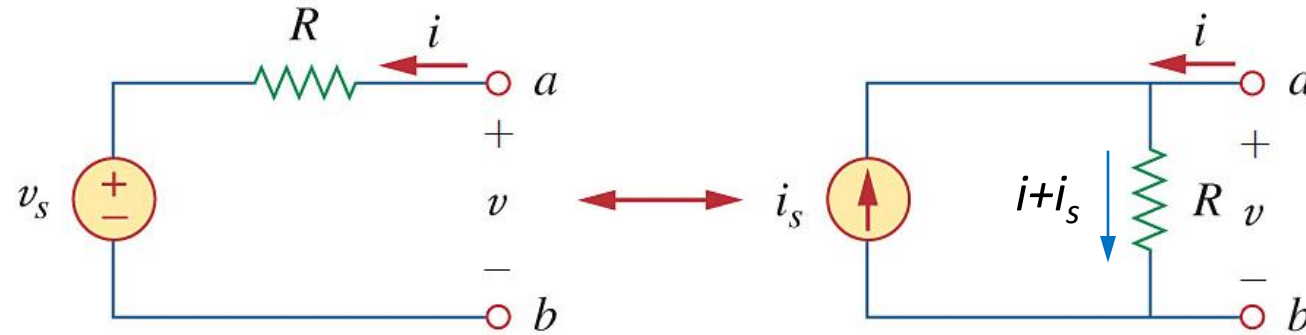


Two circuits are said to be equivalent if they have the same i-v relation.

- Circuit left:  $v = iR + v_s$
- Circuit right:  $v = iR + i_s R$


Two circuits (two iv relations) are identical provided that

$$v_s = i_s R \text{ or } i_s = v_s / R$$

## (i) Voltage source to Current source

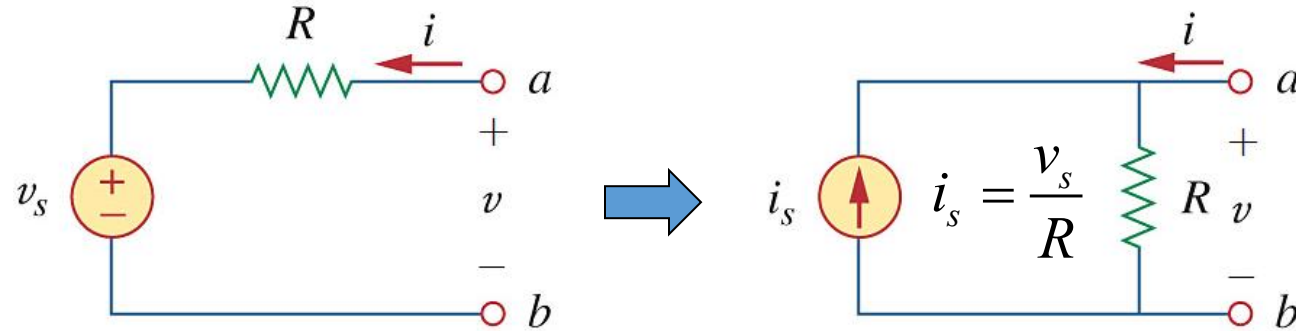


## (ii) Current source to Voltage source

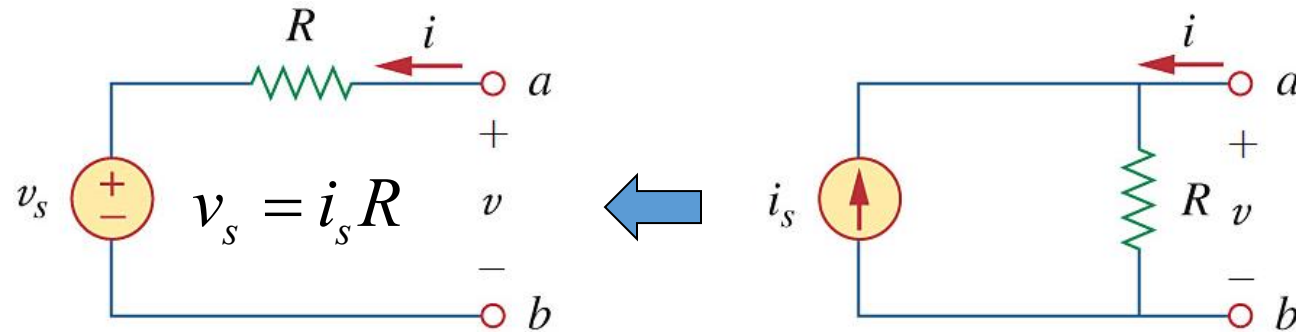

**Be careful about the direction of current source**

- Source transformation also applies to dependent sources, provided we carefully handle the dependent variable.

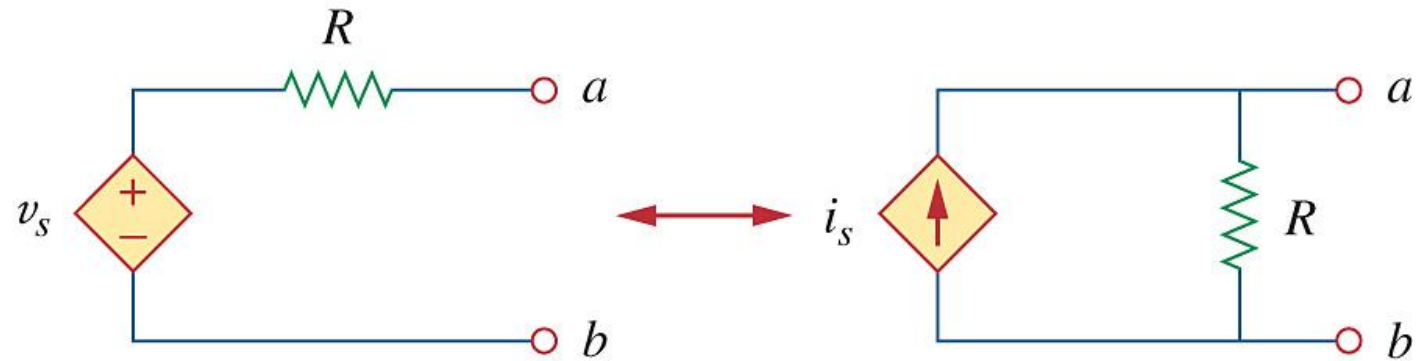

**Example 4.6** Use source transformation to find  $v_o$  in the circuit of Fig. 4.17.


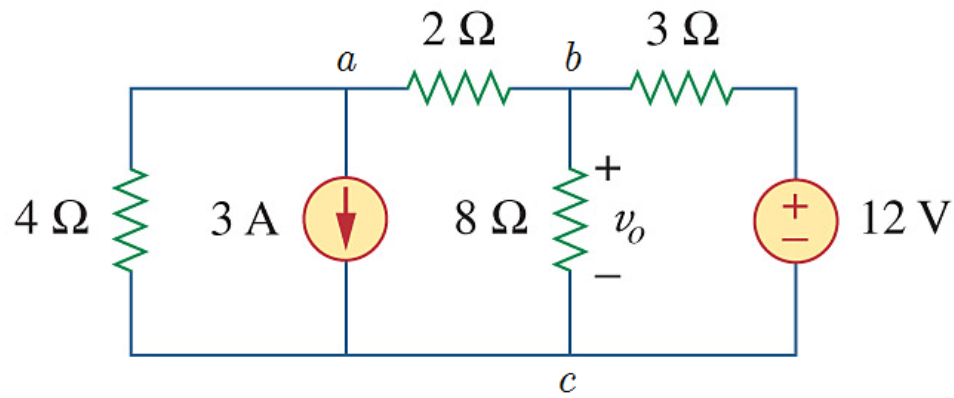



Figure 4.17

$$v_o = 2 \times (8 \parallel 2) = 2 \times \frac{8 \times 2}{8 + 2} = 3.2 \text{ (V)}$$


## Step 1

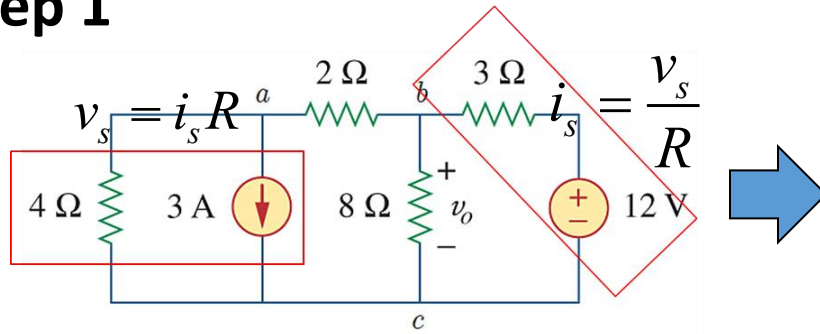


## Step 1

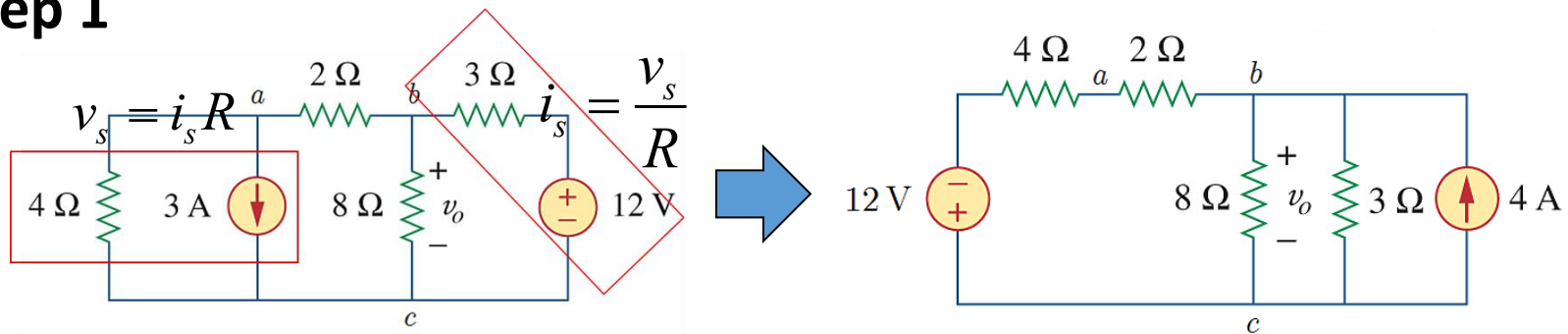


## Step 2

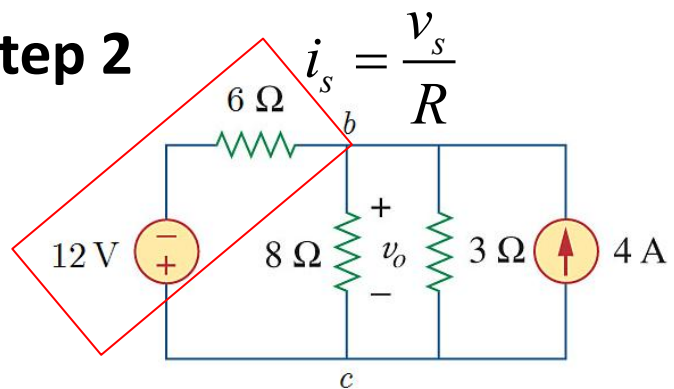


## Step 1

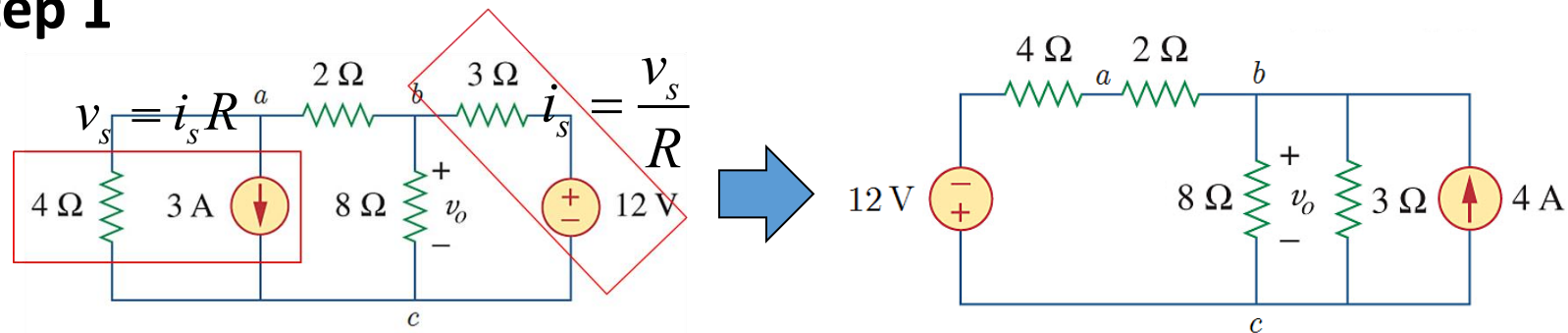


## Step 2

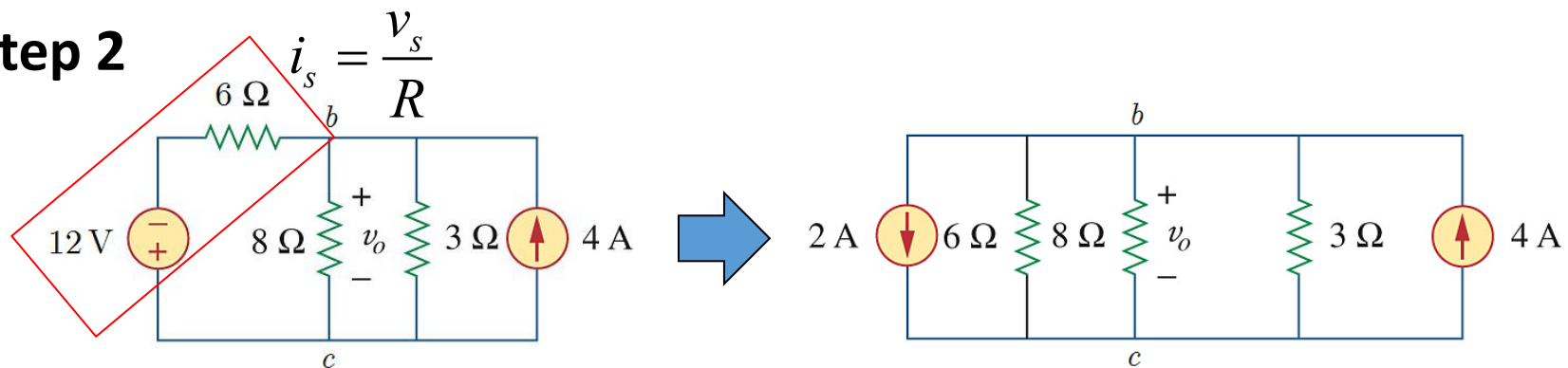


## Step 3

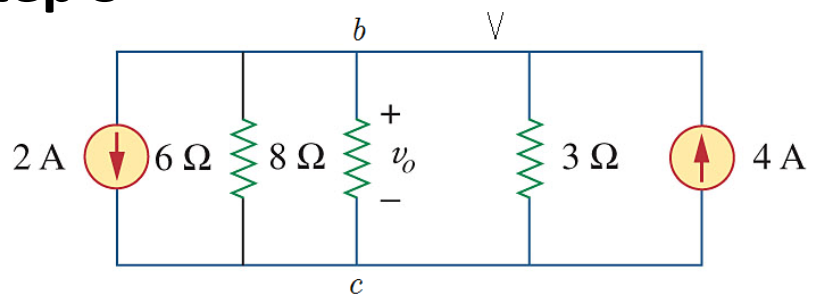


## Step 1

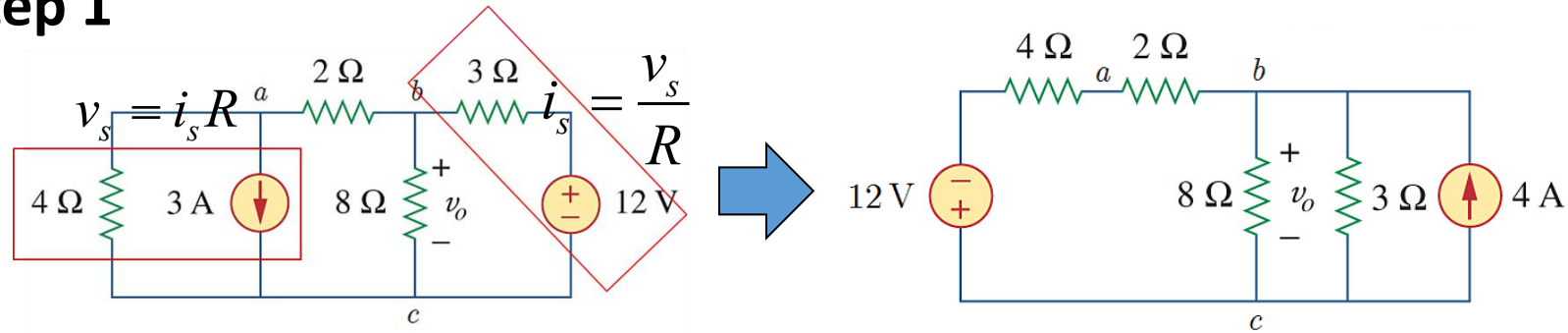

## Step 2

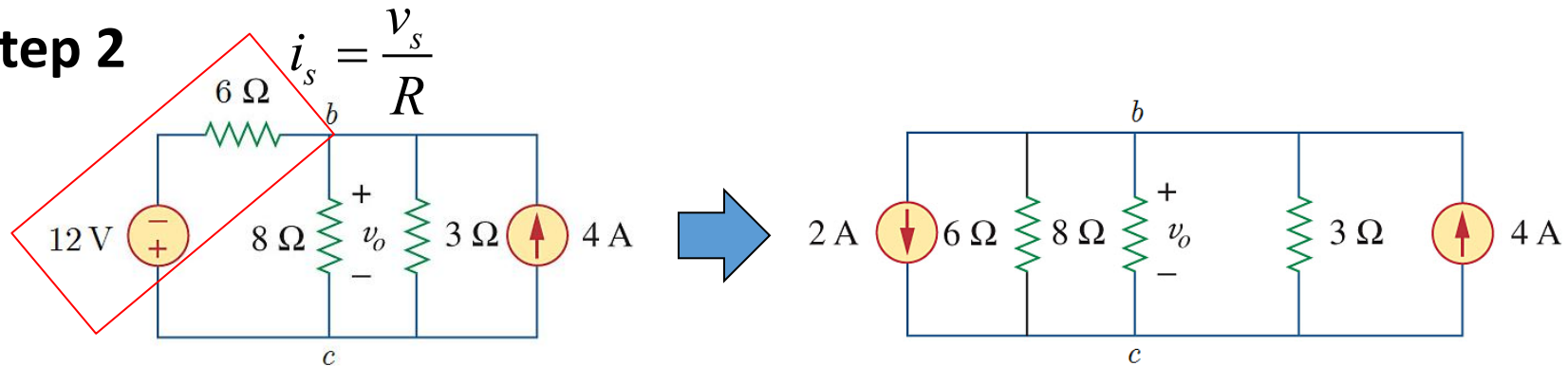

## Step 3

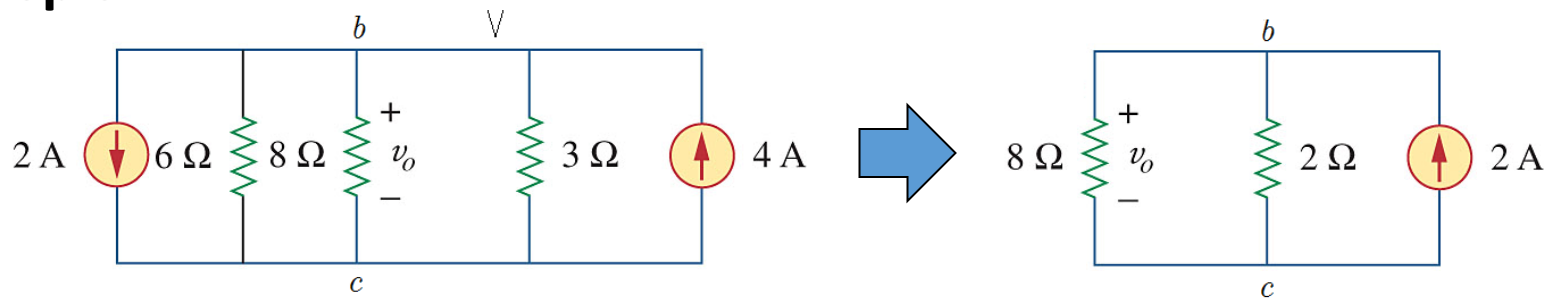



**Practice Problem** Use source transformation to find  $i_x$  in the circuit shown in Fig. 4.22.


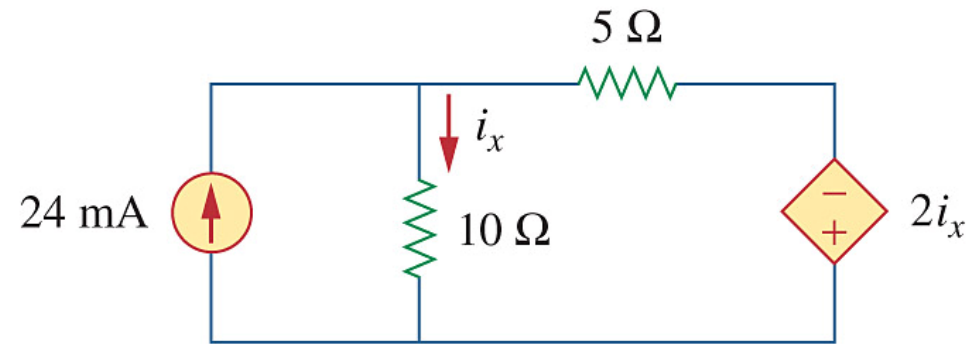


Figure 4.22

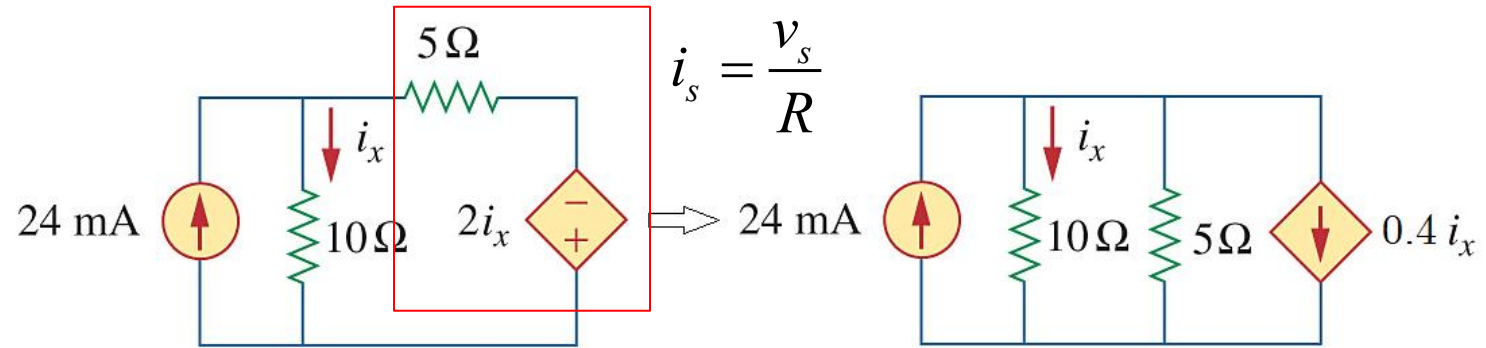


**By KCL**      Current division

$$-24 + i_x + \frac{10i_x}{5} + 0.4i_x = 0$$

$$i_x = \frac{24}{3.4} \approx 7.06 \text{ (mA)}$$

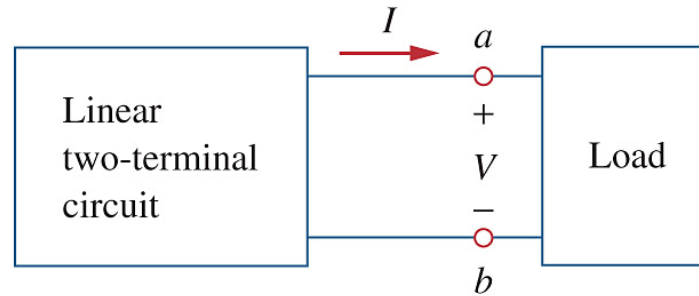
## 4.5 Thevenin's Theorem

- In practice, a particular element in a circuit is variable while other elements are fixed.




- e.g. When we connect a load to a linear two-terminal circuit, we are primarily interested in the **voltage and current at the terminals** of the load.

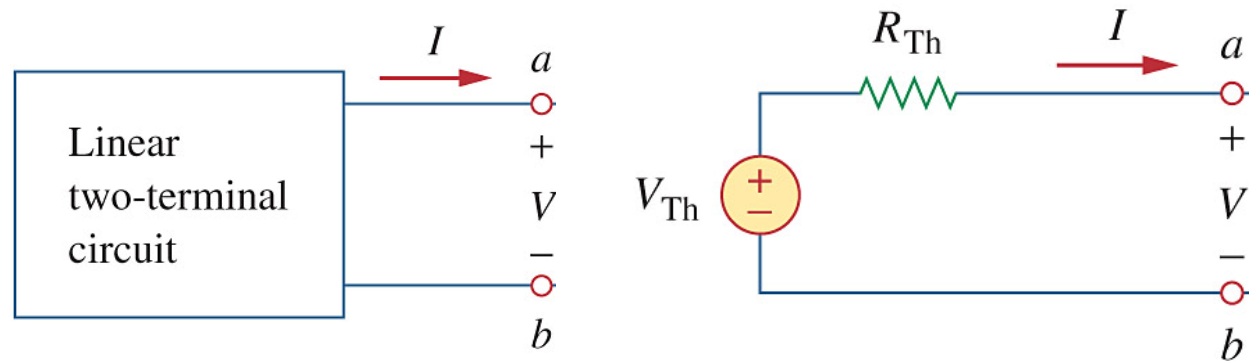- **Thevenin's theorem:** A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$  → a tool of simplifying circuit analysis.



- $V_{Th}$ : open-circuit voltage at the terminals
- $R_{Th}$ : equivalent resistance at the terminals when the independent sources are turned off.

# Proof of Thevenin Equivalent Circuit

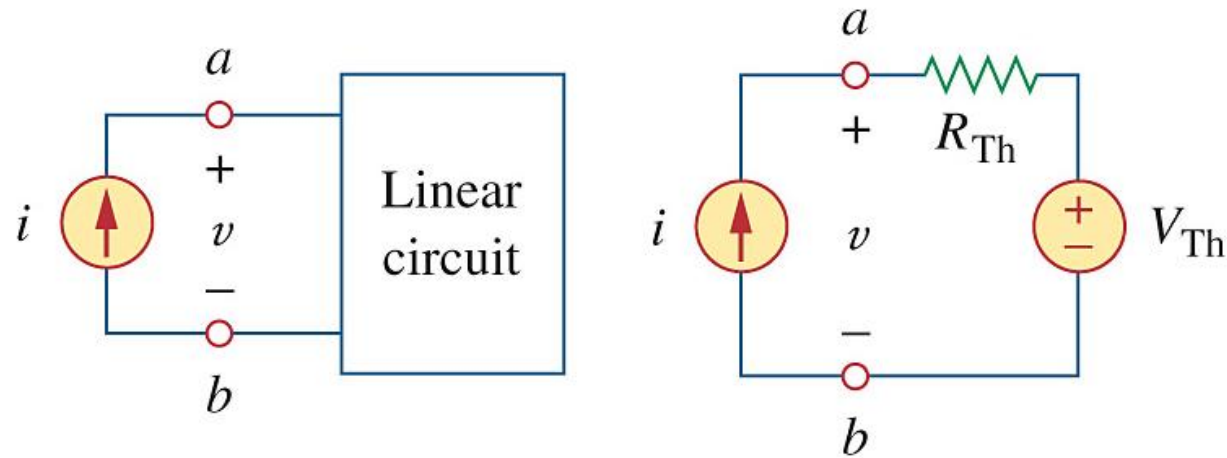


Consider the linear circuit that contains resistors and dependent and independent sources through which **current from an external source** is applied.

Our objective is to ensure that the **voltage-current relation** at terminals  $a$  and  $b$  is **identical to that of the Thevenin equivalent**.

We suppose the linear circuit contains two independent voltage source  $v_{s1}$  and  $v_{s2}$  and two independent current sources  $i_{s1}$  and  $i_{s2}$ .

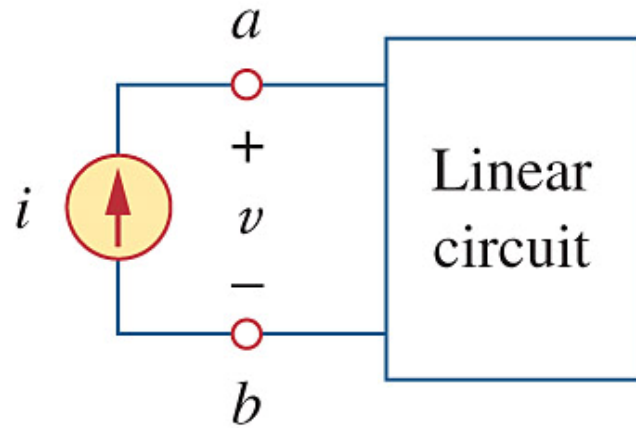By the **superposition**, the terminal voltage  $v$  is



External and internal contributions

$$v = A_0 i + A_1 v_{s1} + A_2 v_{s2} + A_3 i_{s1} + A_4 i_{s2}$$


where  $A_0$ ,  $A_1$ ,  $A_2$ ,  $A_3$ , and  $A_4$  are constants.

$$\text{Let } B_0 = A_1 v_{s1} + A_2 v_{s2} + A_3 i_{s1} + A_4 i_{s2}$$

$$v = A_0 i + B_0$$


$$\text{Let } B_0 = A_1 v_{s1} + A_2 v_{s2} + A_3 i_{s1} + A_4 i_{s2}$$

$$v = A_0 i + B_0$$

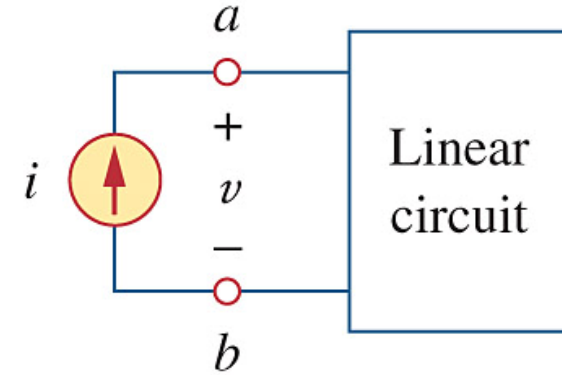

Evaluate the values of constants  $A_0$  and  $B_0$ .

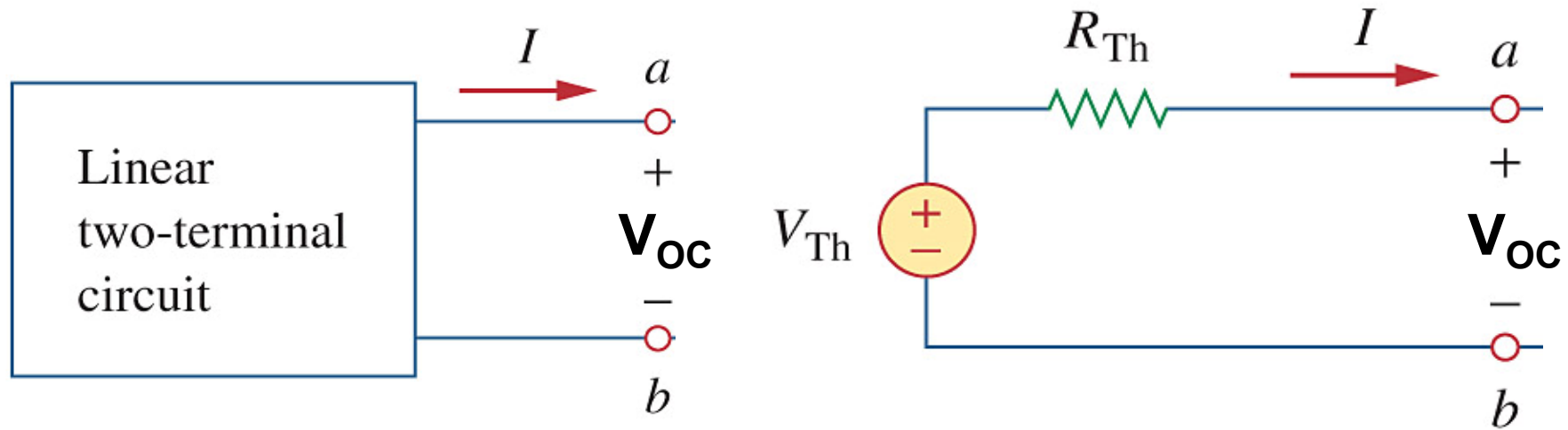- (i) Open Circuit:  $i = 0$  and  $v = v_{oc} = B_0$ , **Contribution from internal sources.**
- (ii) All **internal sources are turned off**,  $B_0 = 0 \rightarrow$  the circuit can be replaced by an equivalent resistance  $\mathbf{R_{eq} = v/i = A_0}$ .



$$B_0 = V_{oc}, \text{ and } V_{oc} = V_{Th}$$


$$A_0 = V_{oc}/I = R_{eq}, \text{ and } R_{eq} = R_{Th}$$

$$\text{Therefore, } v = \mathbf{A}_0 i + \mathbf{B}_0 = \mathbf{R}_{Th} i + \mathbf{V}_{Th}$$



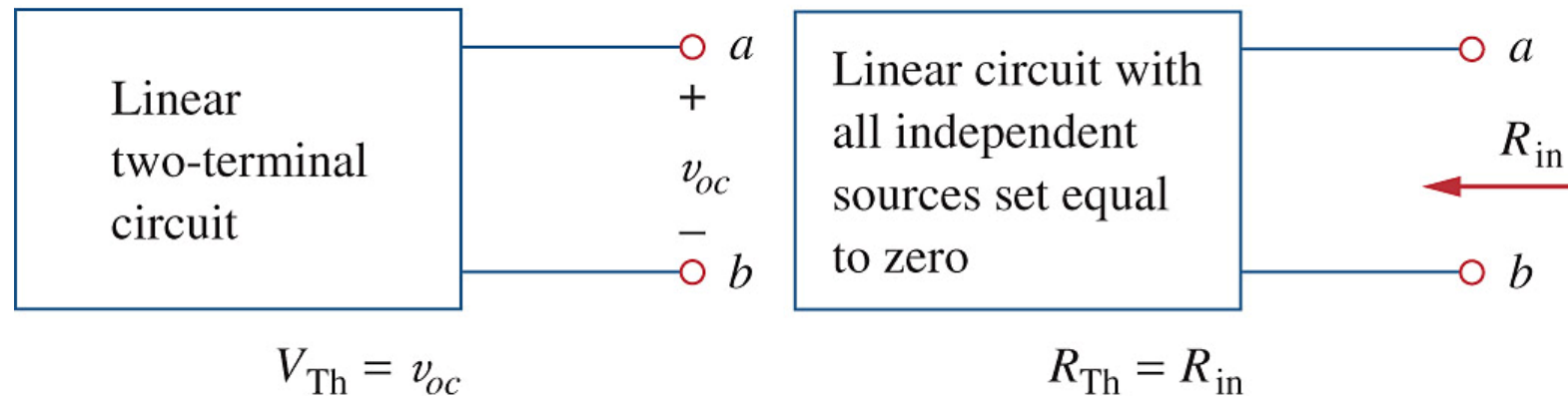
## How to find the Thevenin equivalent circuit

Two circuits are said to be **equivalent** if they have **the same voltage-current relation** at their terminals.




- Make two circuits **open-circuits**  $\rightarrow$  No current flows  $\rightarrow$  **terminal voltage must be equal, i.e.  $V_{Th} = V_{oc}$**
- **Turn off** all the independent sources  $\rightarrow$  the input resistance must be equal, i.e.  **$R_{Th} = R_{in}$**

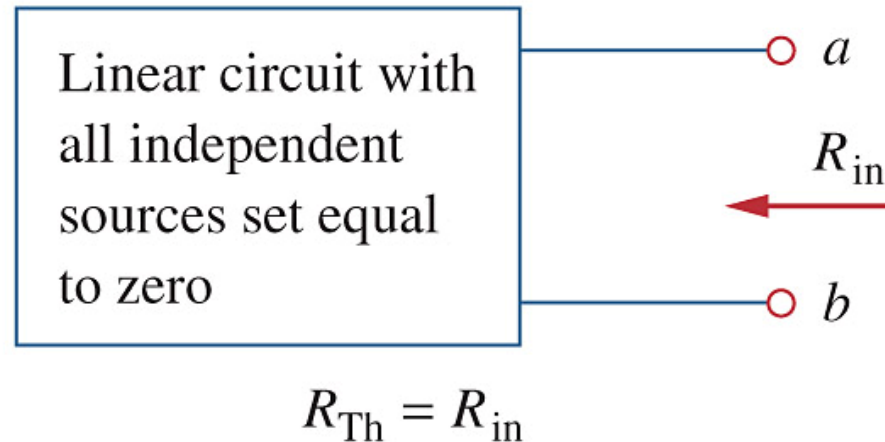To apply this idea in finding the **Thevenin resistance  $R_{Th}$** , we need to consider two cases.



- **Case 1:** If the network has **no dependent sources**, we **turn off all independent sources**.  $R_{Th}$  is the input resistance of the network looking between terminals  $a$  and  $b$ .

- **Case 2:** The network has **dependent sources**. Similar to case 1, we **turn off all independent sources**, but **dependent sources cannot be turned off**.
  - (i) Apply a voltage source  $v_o$  at terminal a and b, and determine the resulting current  $i_o$ . Then,  $R_{Th} = v_o/i_o$
  - (ii) Alternatively, apply a current source  $i_o$  at terminal a-b, and find the terminal voltage  $v_o$ . Again  $R_{Th} = v_o/i_o$

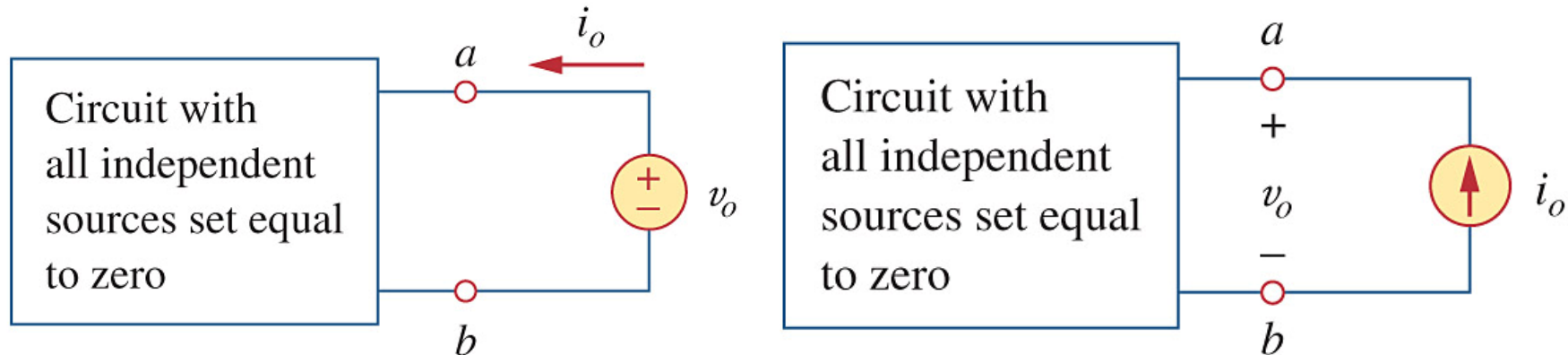

**Example 4.8** Find the Thevenin equivalent circuit of the circuit shown in Fig. 4.27, to the left of the terminals  $a - b$ . then find the current through  $R_L = 6, 16$ , and  $36 \Omega$ .

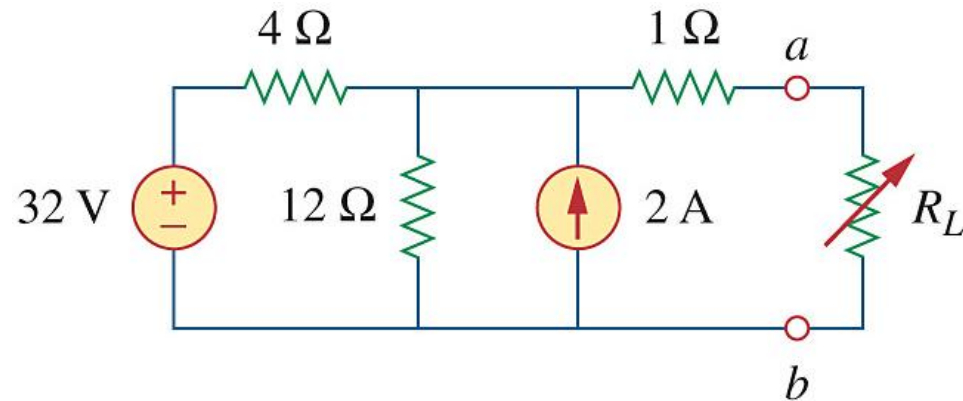


Figure 4.27

(i)  $R_{TH}$

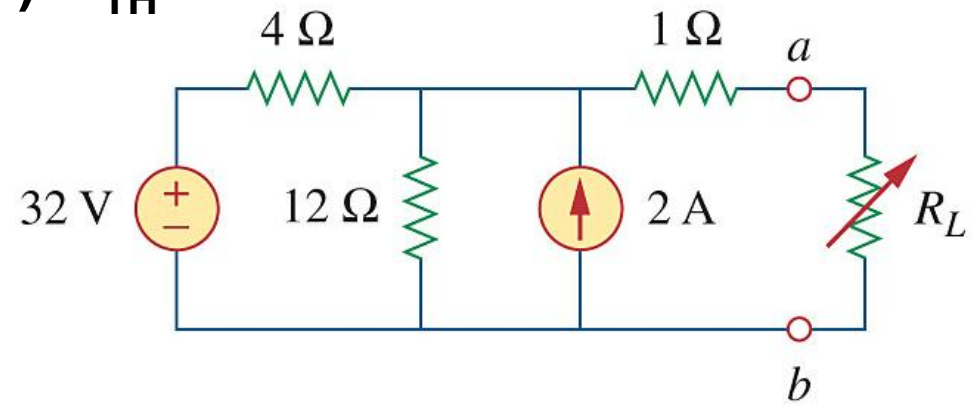


Figure 4.27

(ii)  $V_{TH}$


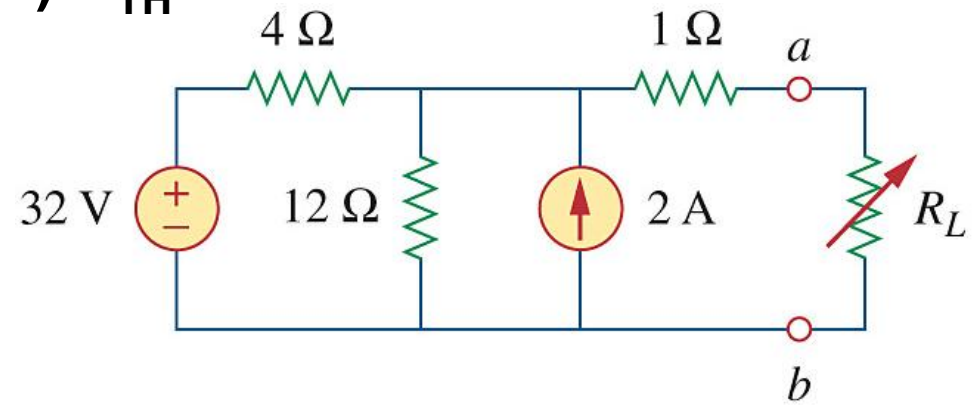


Figure 4.27

(i)  $R_{TH}$

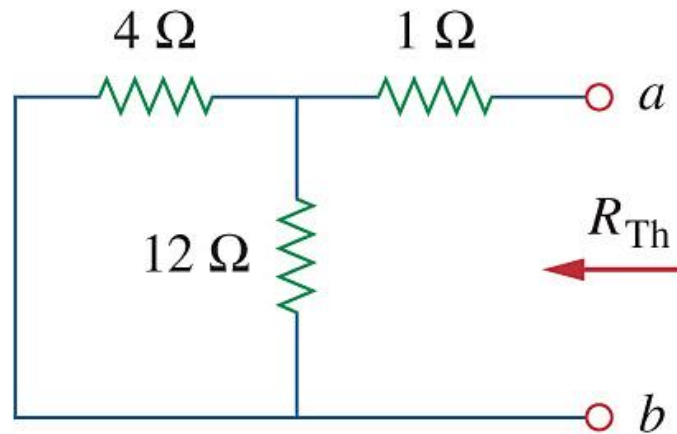


**Voltage source  $\rightarrow$  short**  
**Current source  $\rightarrow$  open**

Turn off all independent sources, the circuit becomes what is shown in Fig. 4.28(a). Thus,

$$R_{Th} = 4 \parallel 12 + 1 = \frac{4 \times 12}{4 + 12} + 1 = 4\ (\Omega)$$


(ii)  $V_{TH}$

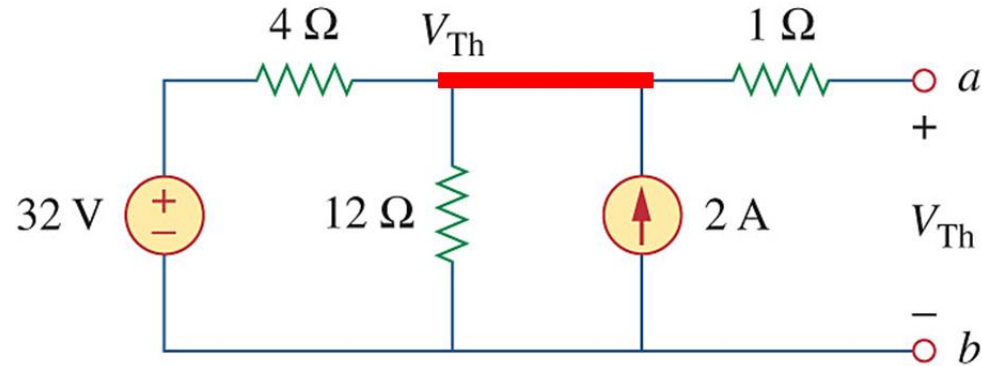


Get  $V_{TH}$  in an open circuit

$$\frac{V_{Th} - 32}{4} + \frac{V_{Th}}{12} - 2 = 0 \Rightarrow V_{Th} = 30 \text{ (V)}$$

**Thevenin Equivalent Circuit**

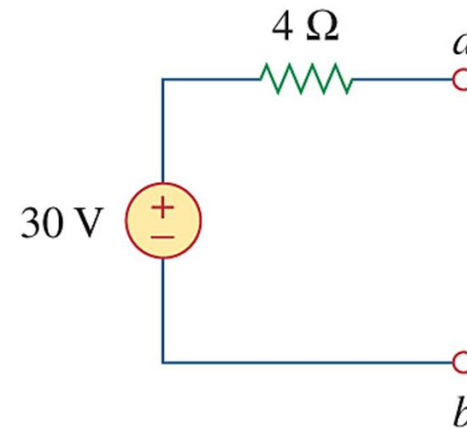



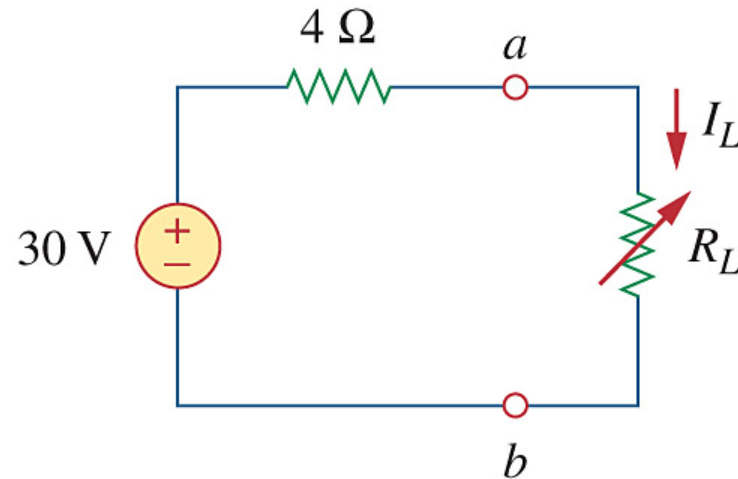


Finally, we can get  $I_L$  by using the Thevenin equivalent circuit

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{30}{4 + R_L} = 3, 1.5, 0.75 \text{ (A)}$$

when  $R_L = 6, 16, 26 \text{ } \Omega$ .

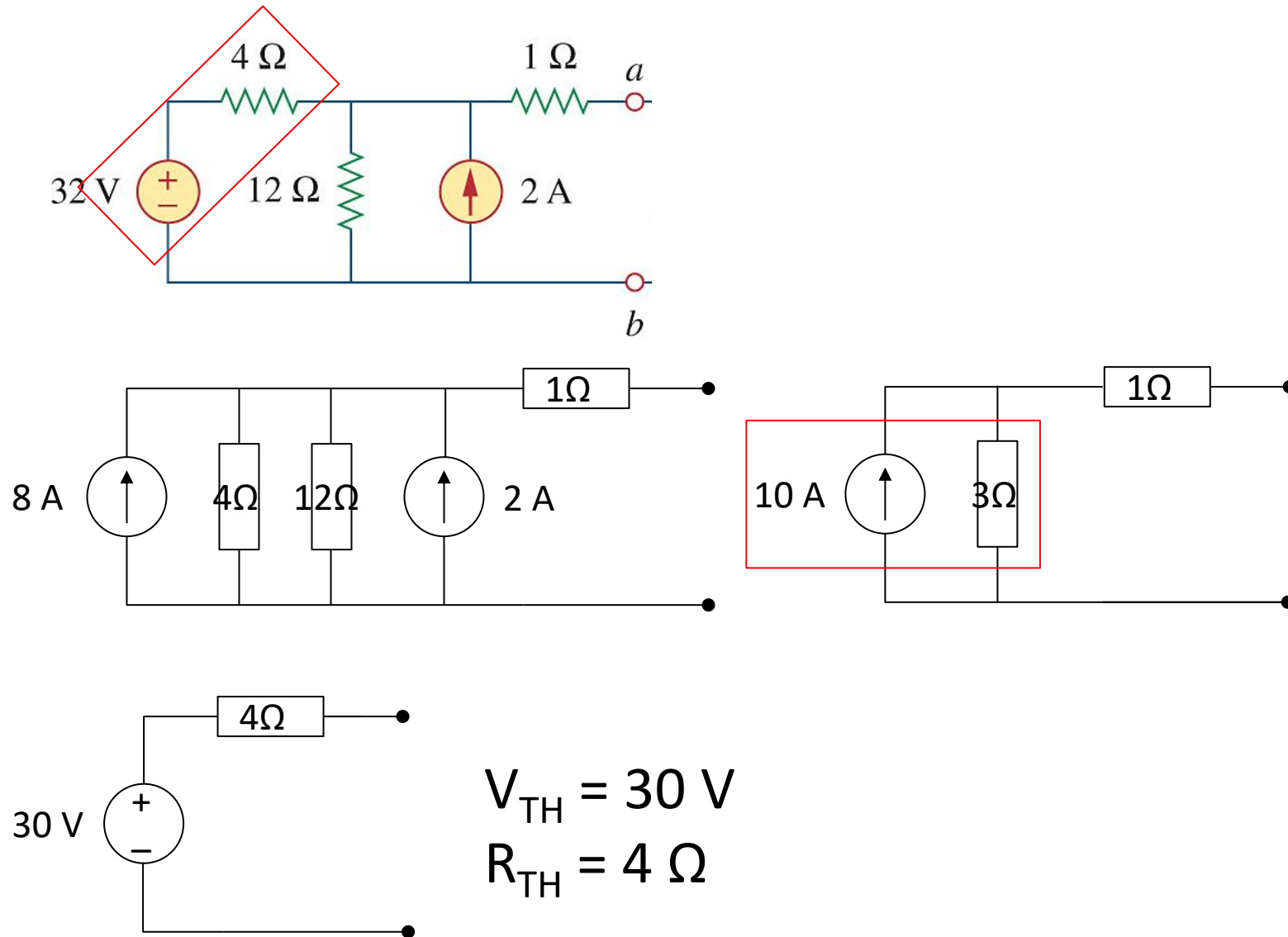Interestingly.. Example 4.8 can be solved by source transformation



**Practice Problem 4.9** Find the Thevenin equivalent circuit of the circuit in Fig. 4.34 to the left of the terminals.



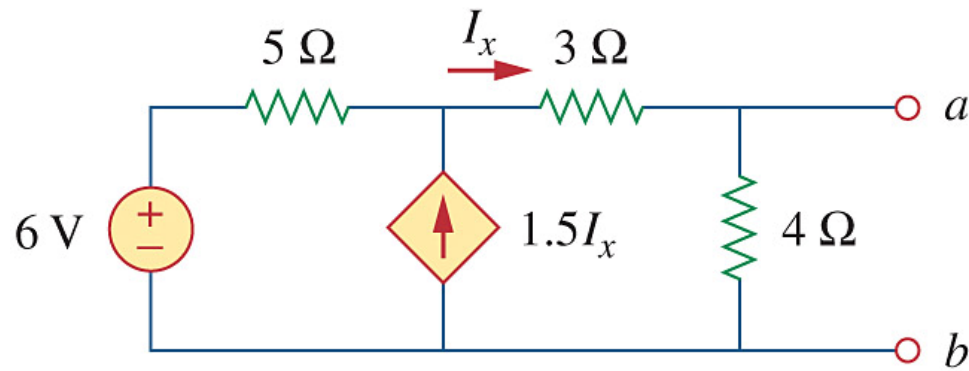


Figure 4.34

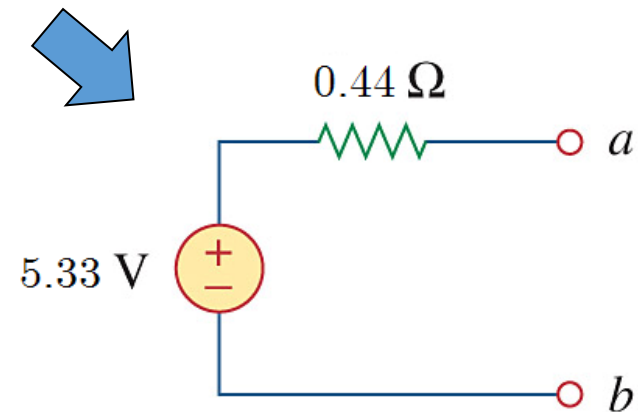

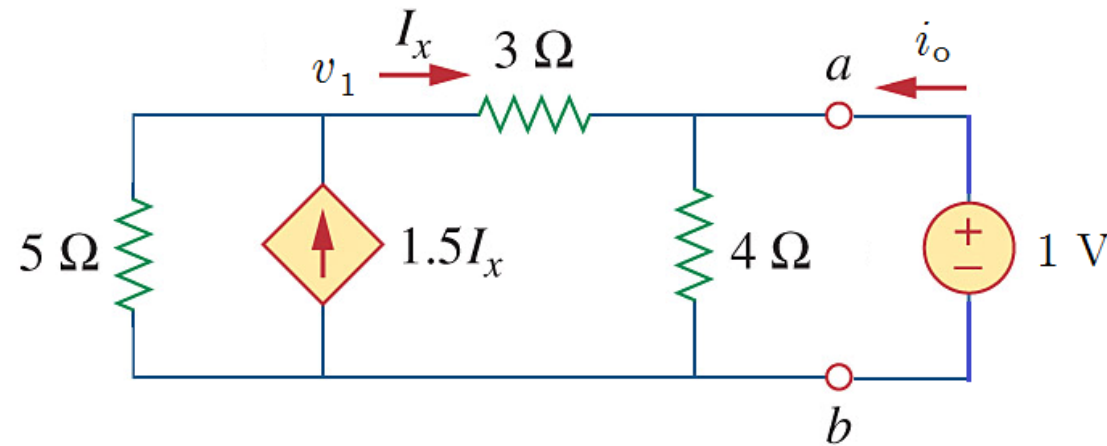
## (i) $R_{Th}$

To find  $R_{Th}$ , first we turn off the independent sources. Because there is a dependent source we apply a test voltage at the terminals a-b.




**\*Note: A test voltage can be any value**


(i)  $R_{Th}$

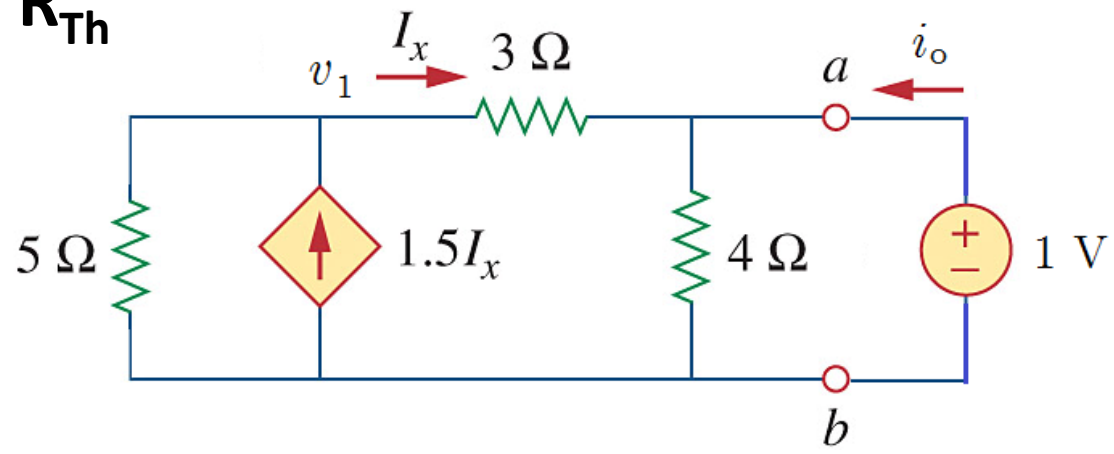

(ii)  $V_{Th}$

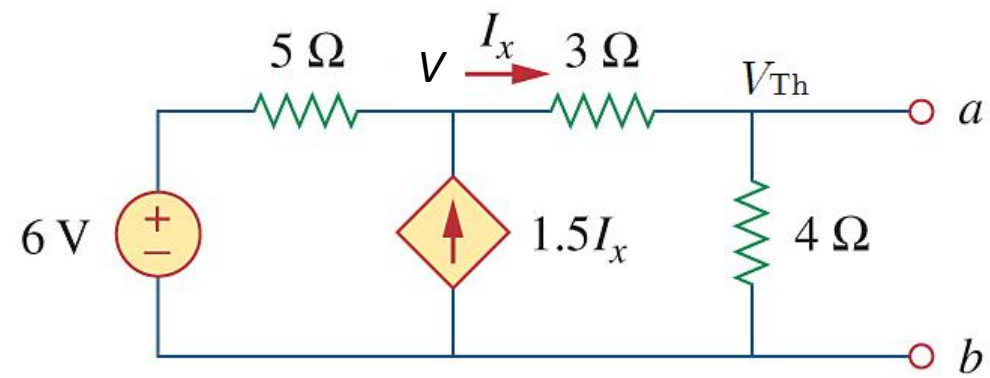

(i)  $R_{Th}$

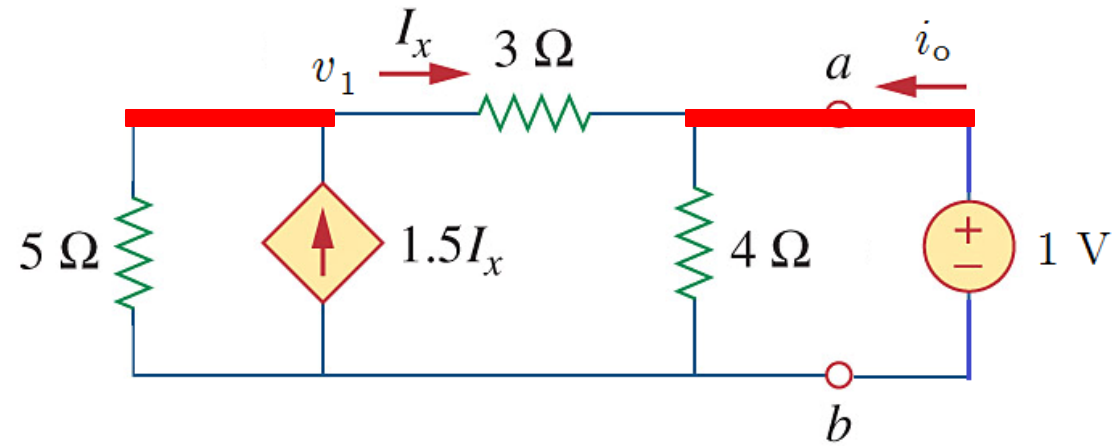


$$\begin{cases} I_x = \frac{v_1 - 1}{3} \\ \frac{v_1}{5} + I_x = 1.5I_x \end{cases} \Rightarrow I_x = -2 \text{ (A)}$$

$$i_o = -I_x + \frac{1}{4} = \frac{9}{4} \text{ (A)}$$

$$R_{Th} = \frac{1}{i_o} = \frac{4}{9} \approx 0.44 \text{ (}\Omega\text{)}$$

(ii)  $V_{Th}$

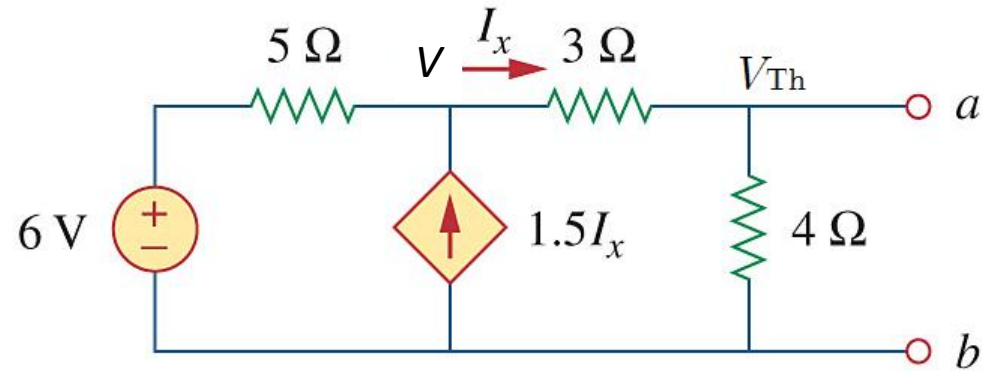

$$(1) \frac{V-6}{5} - 1.5I_x + \frac{V-V_{Th}}{3} = 0$$

$$(2) \frac{V_{Th}-V}{3} + \frac{V_{Th}}{4} = 0 \rightarrow 7V_{Th} = 4V$$

$$(3) I_x = \frac{V-V_{Th}}{3}$$

Put (3) into (1), and then solve the equation

$$V_{Th} = 5.33 \text{ [V]}$$

$$V = 9.33 \text{ [V]}$$

$$I_x = 1.33 \text{ [A]}$$



## Try 10 V test voltage source

**Practice Problem 4.9** Find the Thevenin equivalent circuit of the circuit in Fig. 4.34 to the left of the terminals.



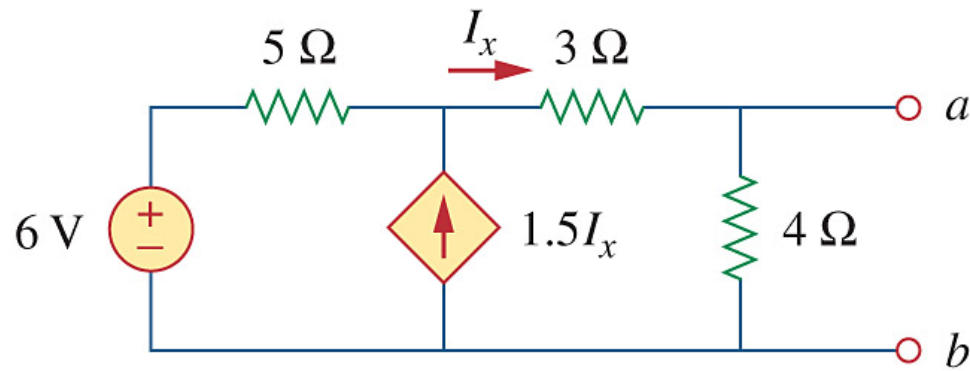


Figure 4.34

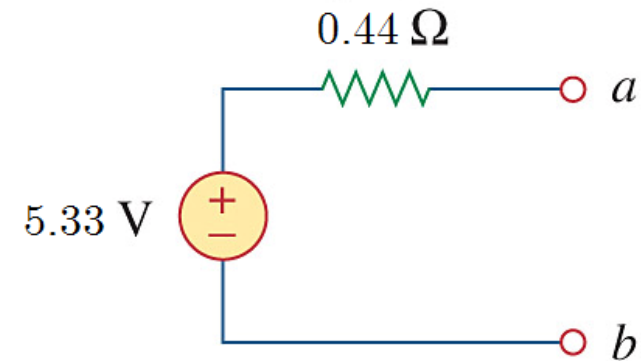

(i)  $R_{Th}$

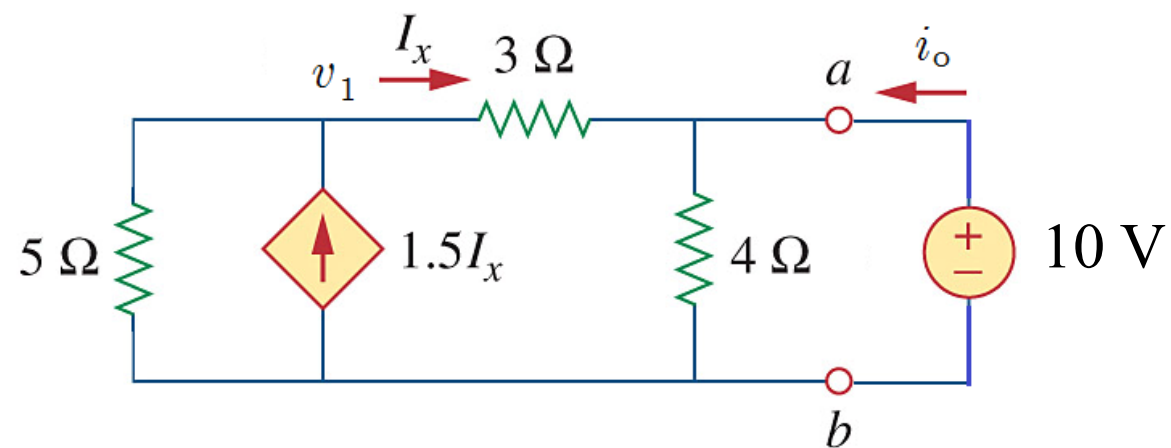

$$\begin{cases} I_x = \frac{v_1 - 10}{3} \\ \frac{v_1}{5} + I_x = 1.5I_x \end{cases} \Rightarrow I_x = -20 \text{ [A]}$$

$$i_o = -I_x + \frac{10}{4} = 22.5 \text{ [V]}$$

$$R_{Th} = \frac{10}{22.5} \approx 0.44 \text{ } (\Omega)$$

**Example 4.10** Determine the Thevenin equivalent of the circuit in Fig. 4.35(a) at terminals  $a - b$ .

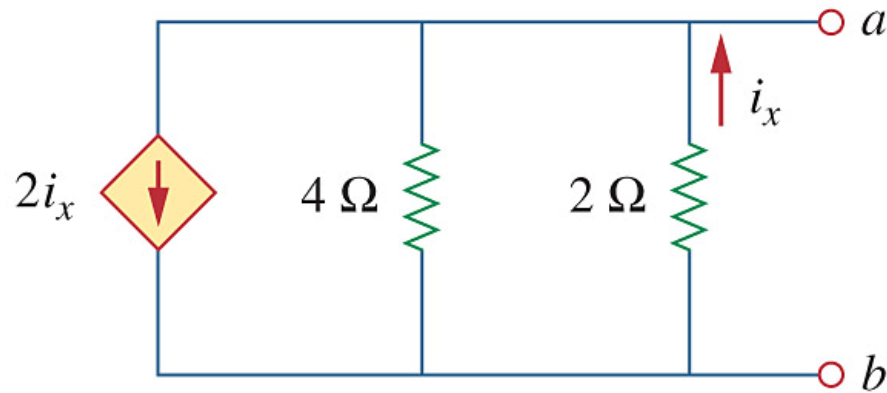


Figure 4.35(a)

(i)  $V_{Th}$

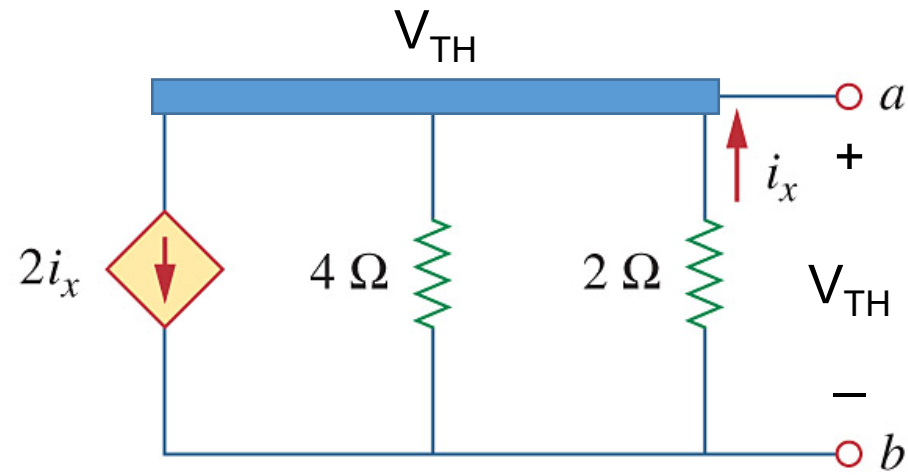


Figure 4.35(a)


Using KCL

$$(1) \frac{V_{TH}}{4} + \frac{V_{TH}}{2} - 2i_x = 0$$

$$(2) i_x = \frac{V_{TH}}{2}$$

$$\rightarrow V_{Th} = 0$$

## (ii) $R_{Th}$

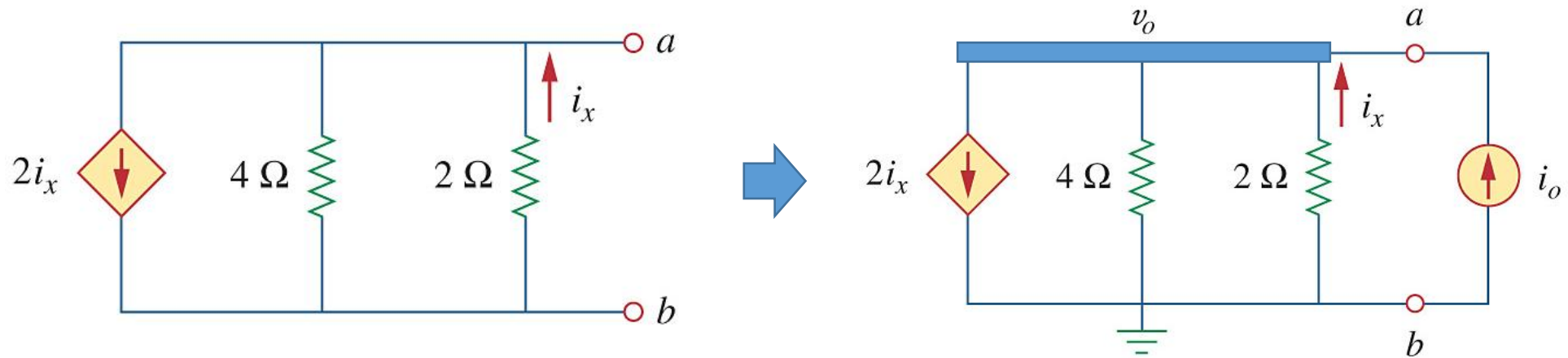

(1) Use a test current source  $i_o$

(2) By KCL at the node  $v_o$

$$2i_x + \frac{v_o}{4} = i_x + i_o$$

$$\Rightarrow v_o = -4i_o$$

(3) By Ohm's law at  $2\Omega$  Resistor

$$v_o = -2i_x$$

$$R_{Th} = \frac{v_o}{i_o} = -4 (\Omega)$$

## $R_{Th}$ with negative value


It often occurs that  $R_{Th}$  takes a negative value. In this case, the negative resistance implies that **the circuit is supplying power**. This is possible in a circuit with dependent sources.

\*It is just an equivalent model and does not mean that there is a resistor (passive) with negative value.
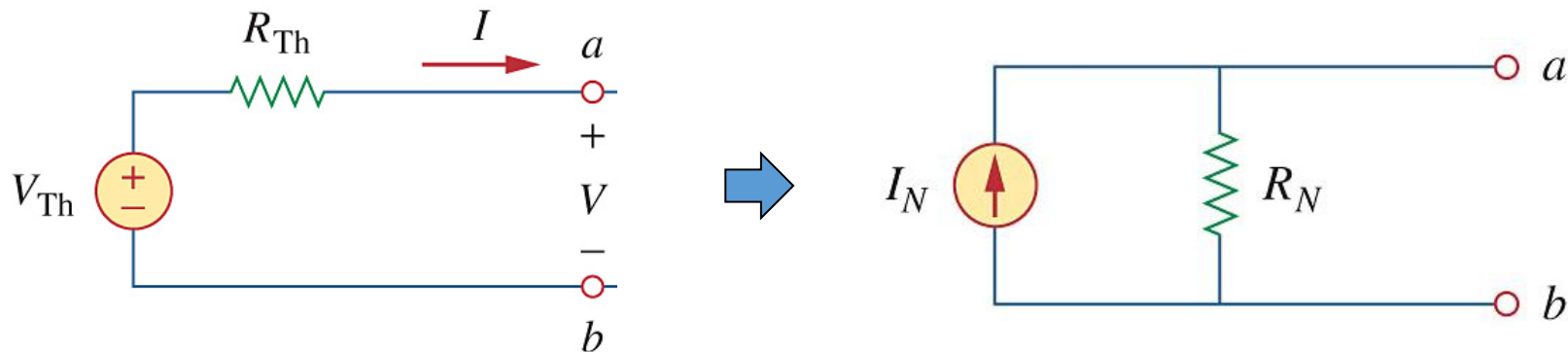
## 4.6 Norton's Theorem


Norton's theorem is similar to Thevenin's theorem.

→ Source transformation of Thevenin's theorem.




**Edward Lawry Norton** (28 July 1898, Rockland, Maine–28 January 1983, Chatham, New Jersey) was an accomplished Bell Labs engineer and scientist famous for developing the concept of the Norton equivalent circuit.

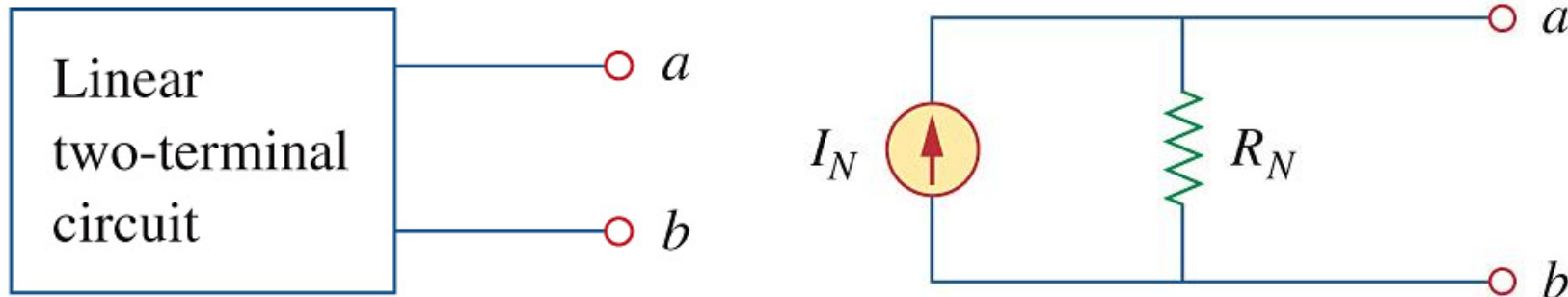**Norton's theorem** states that a linear two-terminal circuit can be replaced by an equivalent circuit **consisting of a current source  $I_N$  in parallel with a resistor  $R_N$** , where  $I_N$  is the short-circuit current through the terminals and  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.





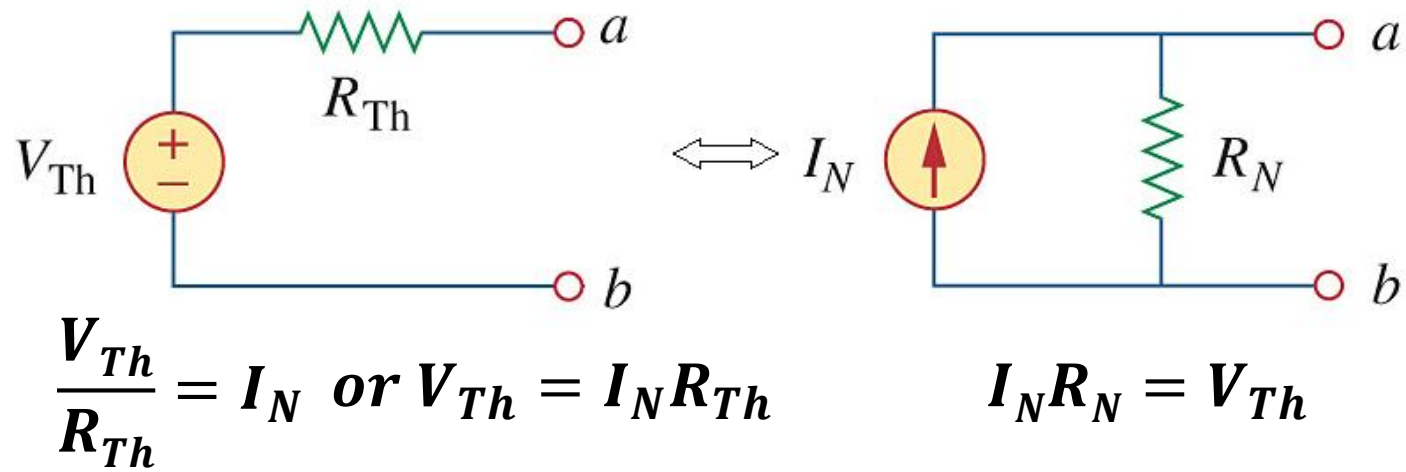We can derive a Norton equivalent circuit from a Thevenin equivalent circuit simply by making a source transformation.



From the Source Transformation,  $\mathbf{R_{Th} = R_N}$  and the Norton current equals the Thevenin voltage divided by the Thevenin resistance  $\mathbf{I_N = \frac{V_{Th}}{R_{Th}}}$

# How to find a Norton equivalent circuit

## (i) $R_N$


- We find  $R_N$  in the same way we find  $R_{Th}$
- In fact, we have just seen that  $R_N = R_{Th}$  by the source transformation.

**Case 1:** If the network has **no dependent sources**, we **turn off all independent sources**.  $R_N$  is the input resistance of the network looking between terminals  $a$  and  $b$ .

**Case 2:** The network has **dependent sources**. Similar to case 1, we **turn off all independent sources**, but **dependent sources cannot be turned off**.
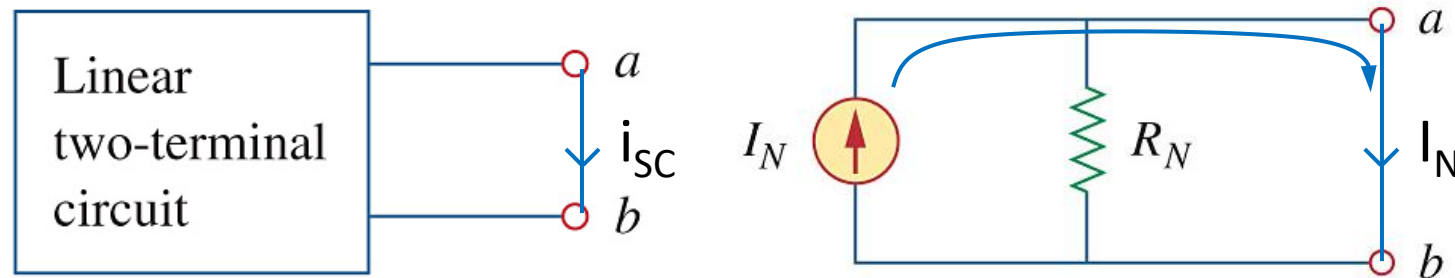
## (ii) $I_N$

To find the **Norton current** we determine **the short-circuit current** flowing from terminal  $a$  to  $b$  in both circuits




Because these two circuits are equivalent, the two currents  $i_{sc}$  and  $I_N$  must be the same.

Therefore,  $i_{sc} = I_N$

Now we found  $R_N$  and  $I_N$  ( $i_{sc}$ )

**Norton Equivalent Circuit** becomes

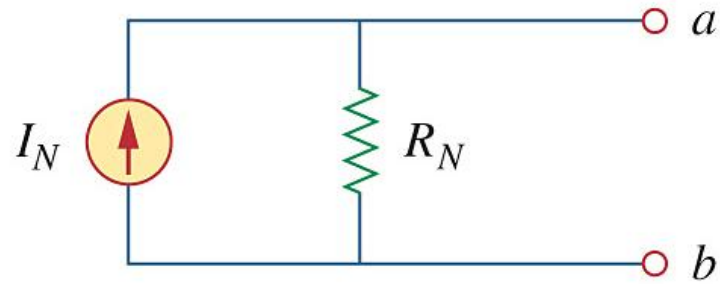


Combining Thevenin and Norton theorems, we have seen that

$$I_N = \frac{V_{Th}}{R_{Th}} \leftrightarrow R_{Th} = \frac{V_{Th}}{I_N}$$

because  $V_{Th} = v_{oc}$

and  $I_N = i_{sc}$

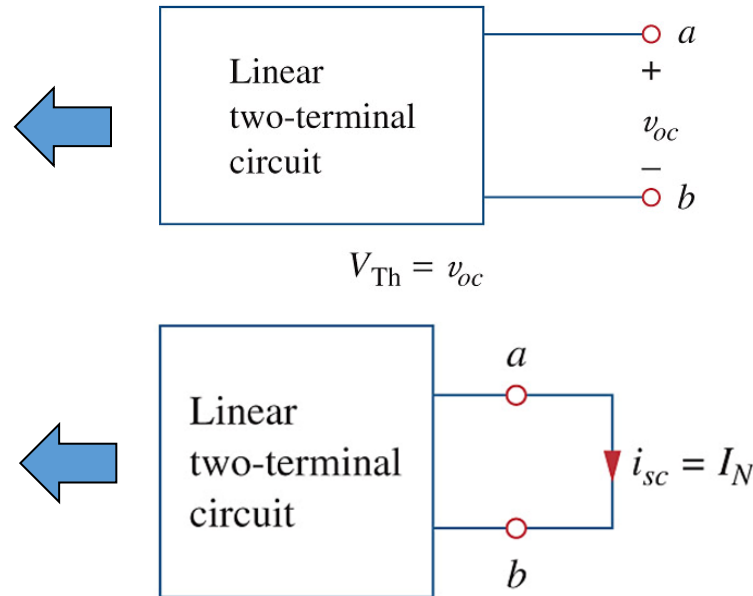

The Thevenin or Norton resistance is the ratio of the open-circuit voltage to the short-circuit current:  $R_{Th} = R_N = \frac{v_{oc}}{i_{sc}}$

**Practice Problem 4.11** Find the Norton equivalent circuit for the circuit in Fig. 4.42, at terminals  $a - b$ .


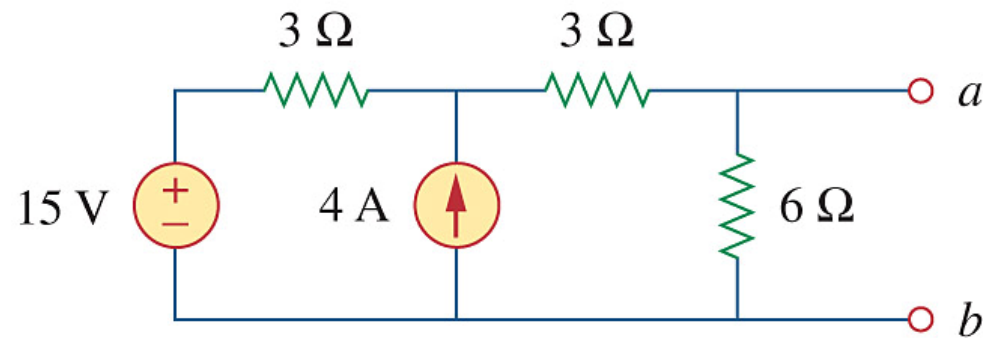


Figure 4.42

(i)  $R_N$

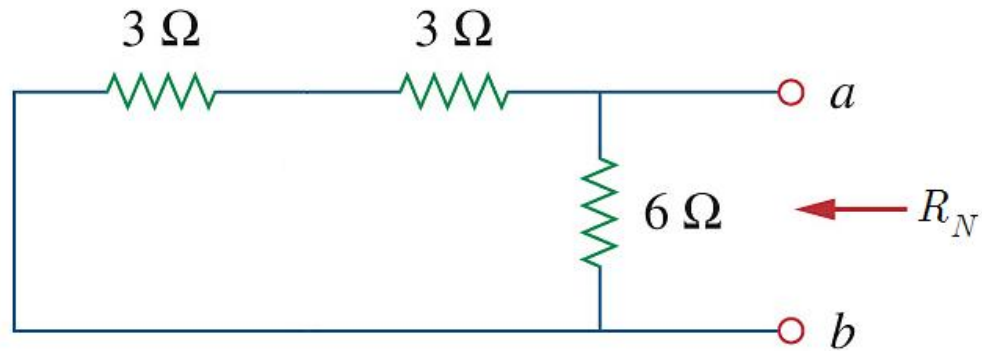


Turn off the voltage and current sources,  
the Norton resistance is

$$R_N = (3 + 3) \parallel 6 = 6 \parallel 6 = 3\ (\Omega)$$

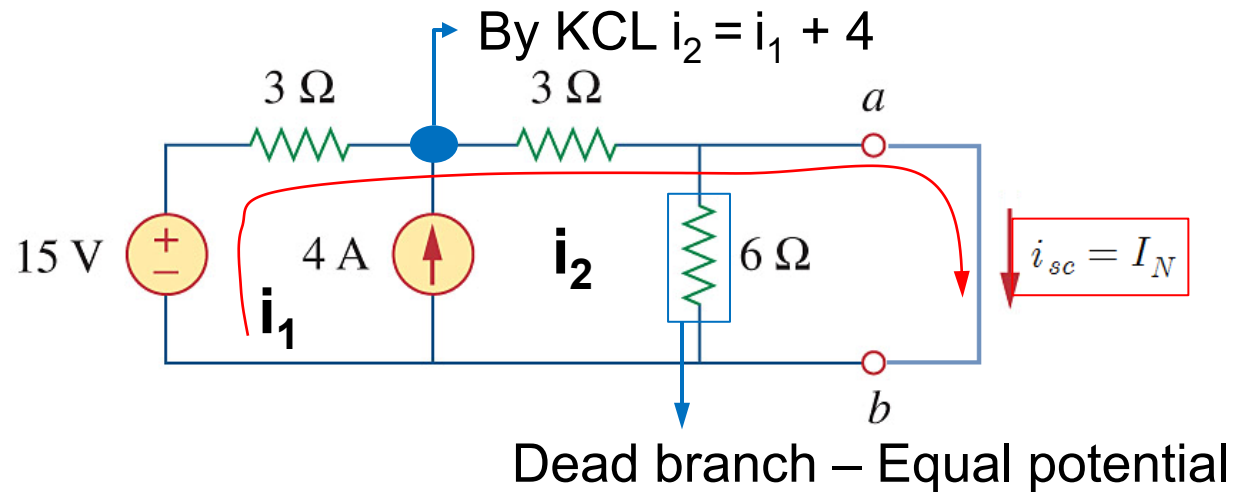(ii)  $I_N$

We short the terminal a-b. Then, we get a circuit



A Supermesh:


$$-15 + 3i_1 + 3(i_1 + 4) = 0 \rightarrow i_1 = 0.5 \text{ [A]}$$

$$i_2 = i_1 + 4 = \mathbf{4.5 \text{ [A]} = I_N}$$



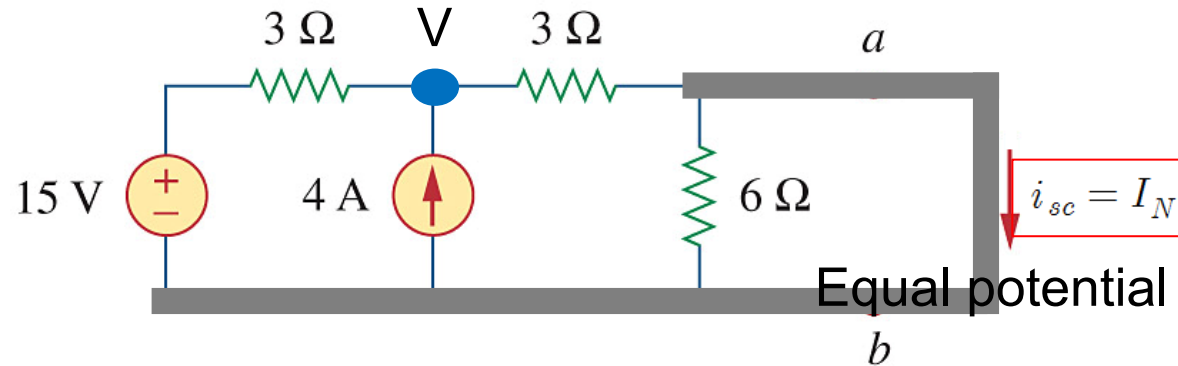(ii)  $I_N$

We short the terminal a-b. Then, we get a circuit



By KCL


$$\frac{V - 15}{3} - 4 + \frac{V}{3} = 0$$
$$V = \frac{27}{2}, i_{sc} = \frac{27}{6} = 4.5\text{ A}$$

We got the parameters for a Norton equivalent circuit


$$R_N = 3 \text{ } [\Omega]$$

$$I_N = 4.5 \text{ } [A]$$

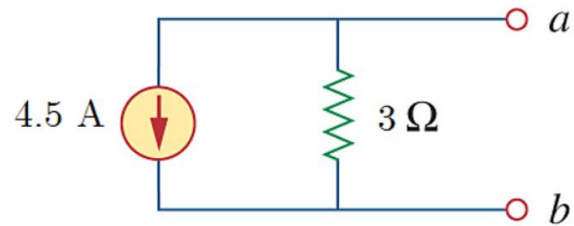Norton equivalent circuit is..? (a) Or (b)?



(a)

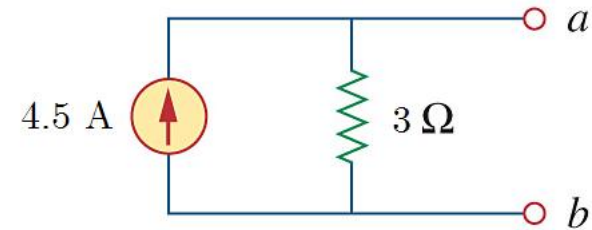

(b)

## 4.8 Maximum Power Transfer

- In many practical situations, a circuit is designed to provide power to a load.
- How can we deliver the **maximum power** to the load?
- **The Thevenin equivalent** is useful in finding the maximum power a linear circuit can deliver to the load.
- Max. Power Transfer = Max. Power Efficiency?

## (i) Maximum power efficiency


Power utility systems are concerned with the generation, transmission, and distribution of large quantities of electric power. This type of systems emphasizes **the efficiency of the power transfer.**

$$\text{Efficiency} = \frac{\text{Useful Power Output}}{\text{Total Power Input}}$$

## (ii) Maximum power transfer

In some cases, for example, communication and electronic systems, the efficiency is not a primary concern. It is often desirable to **transmit as much of power as possible** to the load.
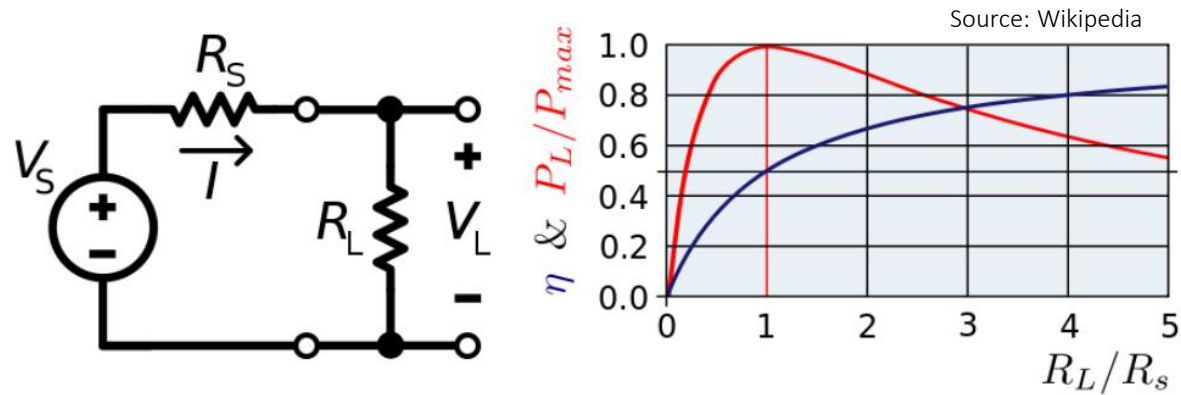
## Maximum power efficiency $\neq$ Maximum power transfer



Efficiency  $\eta$  (*eta*): the ratio of power dissipated by the load,  $R_L$ , to power developed by the source,  $V_S$


$$\eta = \frac{R_L}{R_L + R_S} = \frac{1}{1 + R_S/R_L}$$

- $R_L = R_S$ , then  $\eta = 0.5$
- $R_L \rightarrow \infty$  or  $R_S = 0$ , then  $\eta = 1$
- $R_L = 0$ , then  $\eta = 0$

**The condition of maximum power transfer does not result in maximum efficiency.**

e.g.

### (i) Power utility systems

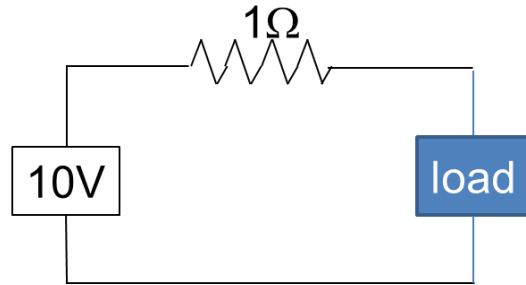

When  $R_L = 9\ \Omega$


Power generated from the source = 10W

Power delivered to the load = 9W

Efficiency of power transfer **90%** (loss=10%)

Care electricity bills
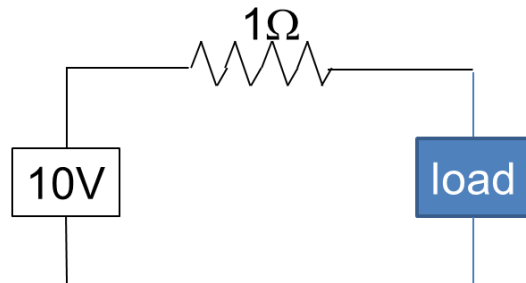
### (ii) Communication & Electronic systems



$R_L = 1\ \Omega$

Power generated from the source = 50W

Power delivered to the load = **25 W**


Efficiency of power transfer 50% (loss=50%)

Care supplying sufficient power

Circuit types	I. Power utility systems	II. Communication & Electronic systems
Power scale	<b>Large quantities</b> of electric power (generation, etc.)	<b>Small amount</b> of power is being transferred
Primary concern	<b>Efficiency</b> of the power transfer	Transmit <b>as much of power as</b> possible to the load



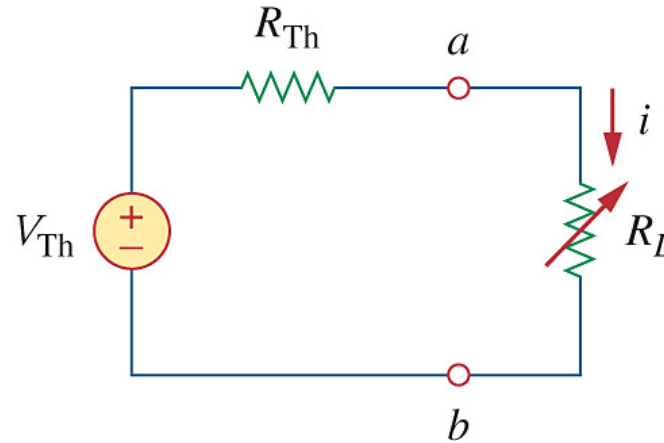
We now consider maximum power transfer in systems.



If the entire circuit is replaced by its Thevenin equivalent except for the load, the power delivered to the load is

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

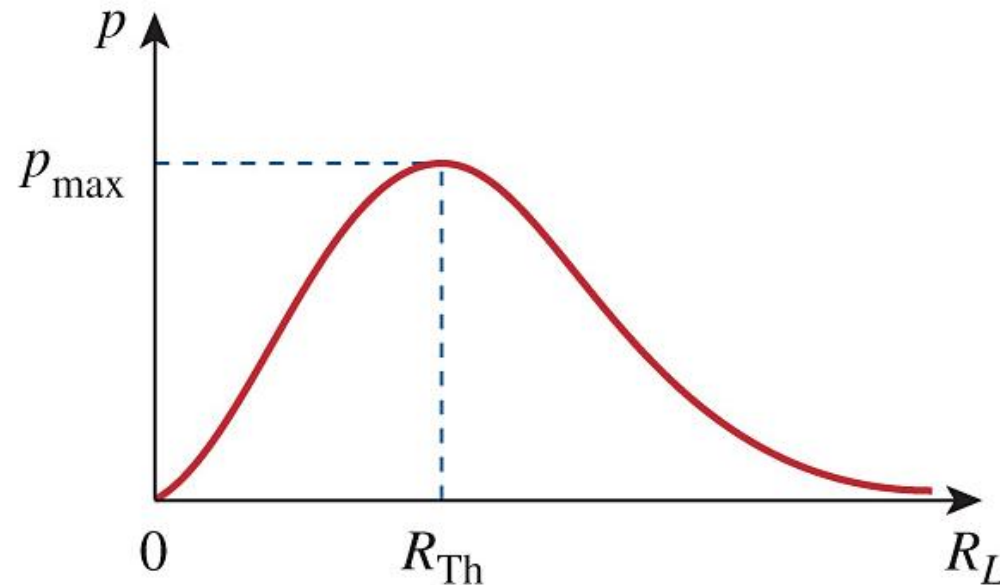The maximum power theorem states that the maximum power is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ( $R_L = R_{Th}$ ).



To prove the maximum power transfer theorem, we differentiate  $p$  with respect to  $R_L$  and set the result equal to zero

$$\frac{dp}{dR_L} = V_{Th}^2 \frac{R_{Th} - R_L}{(R_{Th} + R_L)^3} = 0$$

We have  $R_L = R_{Th}$ .

$$\left. \frac{d^2 p}{dR_L^2} \right|_{R_L=R_{Th}} = V_{Th}^2 \left. \frac{2R_L - 4R_{Th}}{(R_{Th} + R_L)^4} \right|_{R_L=R_{Th}} = -\frac{V_{Th}^2}{8R_{Th}^3}$$

$\left. \frac{d^2 p}{dR_L^2} \right|_{R_L=R_{Th}} < 0$  implies that at  $R_L = R_{Th}$ ,  $p$  takes

the maximum value.

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \quad \text{where } R_{Th} = R_L$$

The maximum power transferred is

$$p_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

It should be noted that delivering the maximum power to the load results in significant internal losses.

**Example 4.13** Find the value of  $R_L$  for maximum power transfer in the circuit of Fig. 4.50. Find the maximum power.

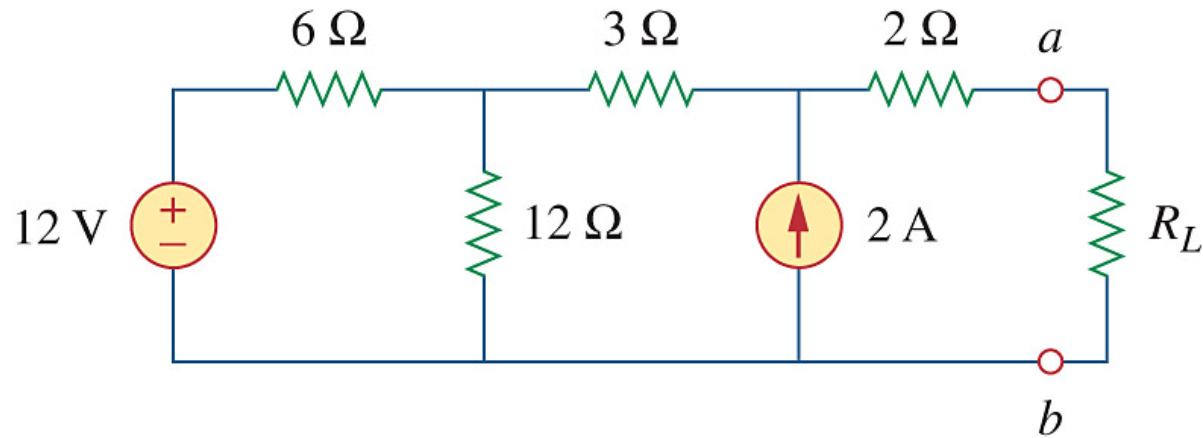


Figure 4.50

First, we will need to find a **Thevenin equivalent circuit**.

(i)  $R_{Th}$

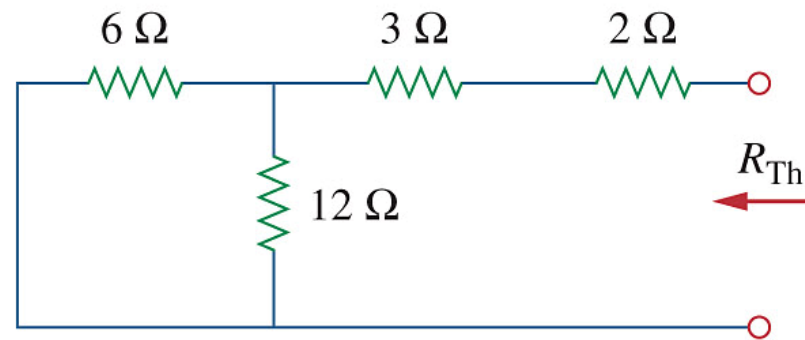


Figure 4.51(a)

First, we will need to find a **Thevenin equivalent circuit**.

(i)  $R_{Th}$


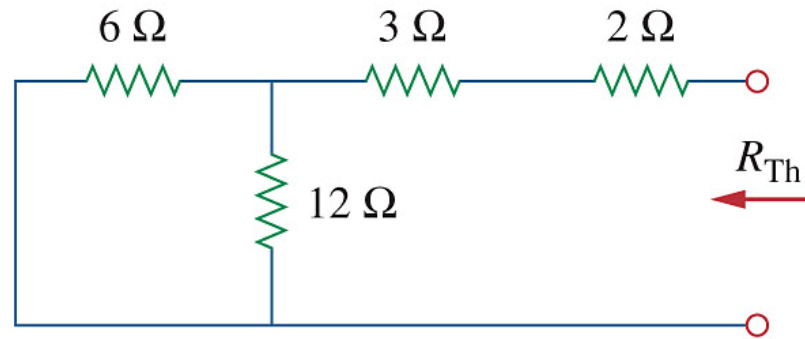



Figure 4.51(a)

$$R_{Th} = 2 + 3 + 6 \parallel 12 = 5 + \frac{6 \times 12}{6 + 12} = 9\ (\Omega)$$

(ii)  $V_{Th}$

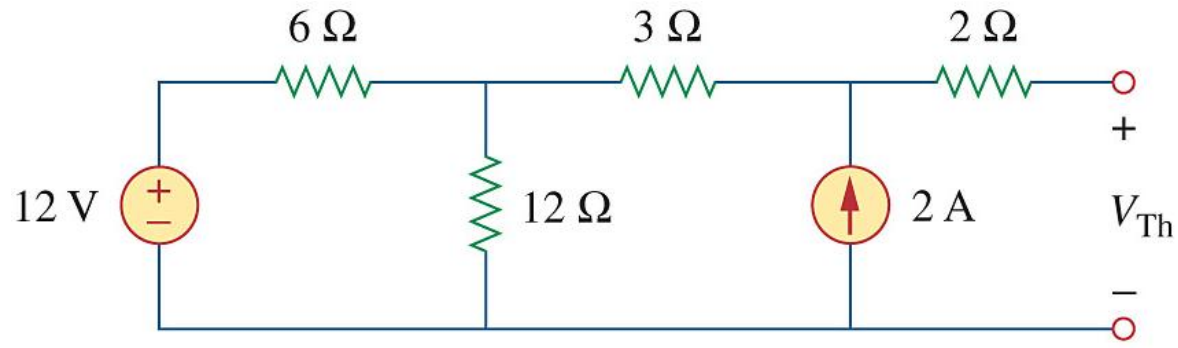


By Source Transformation

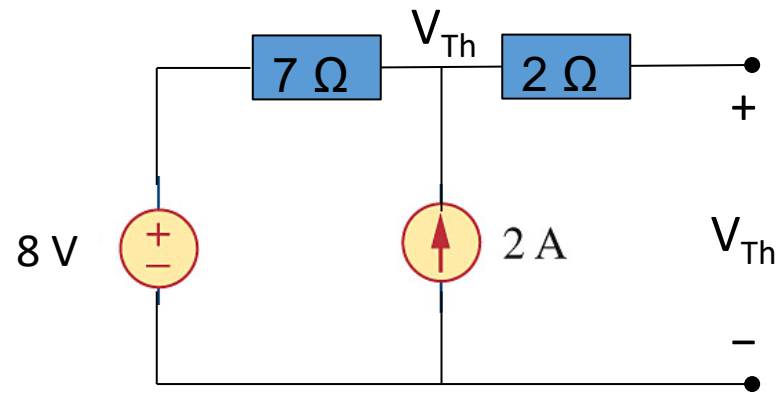




(ii)  $V_{Th}$

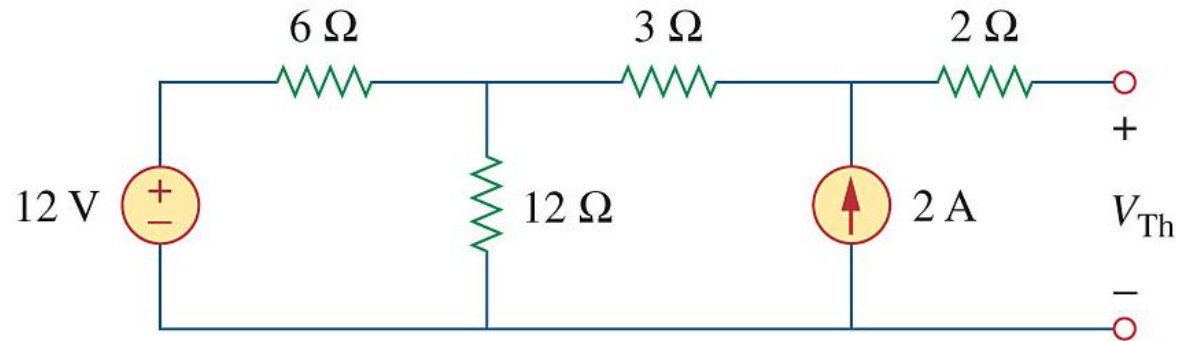

**By Source Transformation**

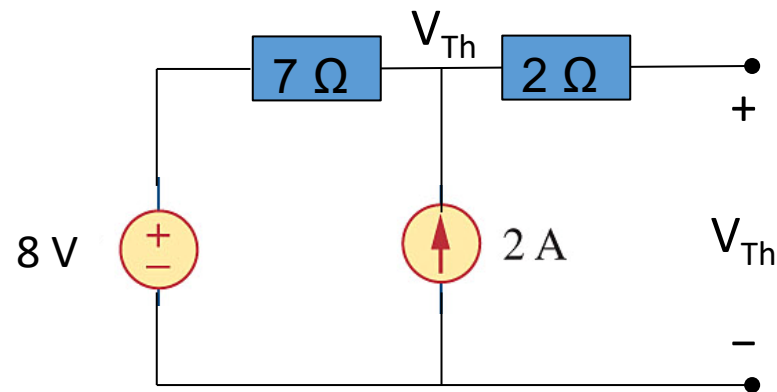


By KCL

$$\frac{V_{Th} - 8}{7} - 2 = 0 \rightarrow V_{Th} = 22 [V]$$

Second, Set  $R_L = R_{Th}$

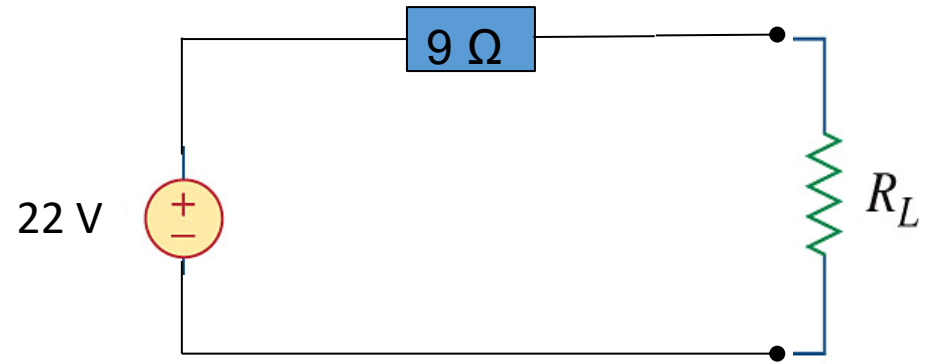And, finally, calculate the maximum power delivered to  $R_L$



If  $R_L = 9 \Omega$ , maximum power will be transferred

$$p_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{22^2}{4 \times 9} = \frac{121}{9} \approx 13.44 \text{ (W)}$$