

Topic 9



Register & Shifter

Introduction

- Two major subsystems in a typical digital system
 - Datapath
 - Datapath **processes, stores, and routes data** according to some control signals generated by controller
 - Controller
 - Controller **generates signals to control datapath components** based on environment event and state of a circuit
- This chapter introduces an important datapath component and simple datapaths


Registers

  - Not new to us...
- Can store data, very common in datapath
- Basic register: external input signals are loaded every cycle




Verilog Modeling of Registers
 
```
module Reg_N_bits (Q, Din, clock);  
  parameter size = 4;  
  input clock;  
  input [size-1:0] Din;  
  output [size-1:0] Q;  
  
  reg Q;  
  
  always @ (posedge clock)  
  begin  
    Q <= Din;  
  end  
endmodule
```



Register with Synchronous Parallel Load

 
- Register loads input signals into the DFFs only when Parallel Load control is active
- Add 2x1 mux to each flip-flop
 - Either existing flip-flop value, or new value to load



Synchronous active high Load

Verilog Modeling of Registers
 
```
module Reg_N_bits (Q, Din, clock, load);  
    parameter size = 4;  
    input clock, load;  
    input [size-1:0] Din;  
    output [size-1:0] Q;  
  
    reg Q;  
  
    always @ (posedge clock)  
    begin  
        if (load) Q <= Din;  
    end  
endmodule
```



Incomplete **if** statement, but OK, why?

Verilog Testbench for Register

```
module Test_Banch;
    parameter half_period = 50;
    parameter reg_size = 3;

    wire [reg_size-1:0] Q;
    reg [reg_size-1:0] Din;
    reg                clock, load;


    Reg_N_bits #(reg_size) UUT (Q, Din, clock, load);

    initial begin
        #0    clock = 0; Din = 0;
        #200 Din = 5; load = 1;
        #100 load = 0;
        #200 Din = 3;
        #200 load = 1;
    end


    always #half_period clock = ~clock;

    initial #1000 $stop;
endmodule
```

Timing Diagram from Simulation

 


N-bit Mux Example

 


- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) -- each is 8-bits wide
 - Choose which to display using two inputs x and y
 - Use 8-bit 4x1 mux

Register Example: Above-Mirror Display

 


 - Four simultaneous values from car's computer: Temperature, Average mpg, Instantaneous mpg, Millage remaining
- To reduce wires: Computer writes only 1 value at a time, loads into one of the four registers selected by decoder




Register Files

 - ***MxN register file*** provides efficient access to M N-bit-wide registers
 - If we have many registers but only need access one or two at a time, a register file is more efficient
 - Ex: Above mirror display (earlier example), but this time having 16 32-bit registers
 - Too many wires, and big mux is too slow




Register File

- Packing the registers together

 



Register-File Example: Above-Mirror Display

 - Four 32-bit registers that can be written by car's computer, and displayed
 - Use 4x32 register file
 - Simple, elegant design
- Register file hides complexity internally
 - And because only one register needs to be written and/or read at a time, internal design is simple



Expected Behavior of Register File

  - May be designed to write one register and read one register in one clock cycle (Operation on the same register)



Verilog Modeling of Clocked Register File

```
module memory (R_data, W_data, W_addr, R_addr, W_en, R_en, clock);  
  parameter width = 32;  
  parameter addr_width = 2;  
  parameter number = 2**addr_width;  
  
  output [width-1:0] R_data;  
  input [width-1:0] W_data;  
  input [addr_width-1:0] W_addr, R_addr;  
  input W_en, R_en, clock;  
  
  reg [width-1:0] R_data;  
  reg [width-1:0] memory [number-1:0];  
  
  always @(R_en, R_addr, memory) begin  
    R_data = 'bz;  
    if (R_en) R_data = memory[R_addr];  
  end  
  
  always @(posedge clock)  
    if (W_en) memory[W_addr] = W_data;  
endmodule
```

Testbench for RF

```
module test_RF;
  parameter width = 32, addr_width = 2, number = 2**addr_width;
  parameter duty_c = 20, period = 100;
  reg [width-1:0] W_data;
  reg [addr_width-1:0] W_addr, R_addr;
  reg W_en, R_en, clock;
  wire [width-1:0] R_data;


  memory UUT (R_data, W_data, W_addr, R_addr, W_en, R_en, clock);

  initial begin
    #0 clock=0; W_data=0; W_addr=0; R_addr=0; W_en=0; R_en=0;
    #100 W_data=9; W_addr=3; W_en=1; #100 W_data=22; W_addr=1; W_en=1;
    #100 W_en=0; R_en=1; R_addr=3; #100 R_en = 0;
    #100 W_data=177; W_addr=2; W_en=1; #50 R_addr=1; R_en=1;
    #50 W_data=555; W_addr=3; #50 R_addr=3;
  end

  always begin #(period-duty_c) clock=~clock; #duty_c clock=~clock; end


  initial #1000 $stop;
endmodule
```


Simulation Results

 


Shift Register

 - One type of register
 - Stores binary data
 - Stored data can be shifted right (MSB >> LSM) or left (MSB << LSB)
 - Example: Shift right per clock edge



Shift Register

 - Implementation:
 - Connect Q output of one flip flop to the D input of the next flip flop
 - 4-bit shift register



	IN	OUT(3:0)
Initial value:	0	0110
rising edge:	0	0011
rising edge:	0	0001
rising edge:	0	0000
rising edge:	1	1000
rising edge:	0	0100

Verilog Modeling of Shift Registers

```
module Shift_Reg (Q, Dout, Din, clock);  
  input clock, Din;  
  output Dout;  
  output [3:0] Q;  
  
  reg [3:0] Q;  
  
  always @ (posedge clock)  
  begin  
    Q[2:0] <= Q[3:1];  
    Q[3]    <= Din;  
  end  
  
  assign Dout = Q[0];  
endmodule
```

Verilog Testbench for Shift Registers

```
module Test_Bench;
    parameter half_period = 50;
    wire [3:0] Q;  wire Dout;  reg  Din, clock;

    Shift_Reg UUT (Q, Dout, Din, clock);

    initial begin
        $display("*****");
        $display("The textual simulation results:");
        $display("*****");
        $monitor($time, "clock = %d  Din = %b  Q = %b  Dout = %d",
            clock, Din, Q, Dout);
    end

    initial begin
        #0    clock = 0; Din = 0;
        #300  Din = 1;
        #400  Din = 0;
    end

    always #half_period clock = ~clock;

    initial #1000 $stop;
endmodule
```


Textural Simulation Result

The textual simulation results:

0	clock = 0	Din = 0	Q = xxxx	Dout = x
50	clock = 1	Din = 0	Q = 0xxx	Dout = x
100	clock = 0	Din = 0	Q = 0xxx	Dout = x
150	clock = 1	Din = 0	Q = 00xx	Dout = x
200	clock = 0	Din = 0	Q = 00xx	Dout = x
250	clock = 1	Din = 0	Q = 000x	Dout = x
300	clock = 0	Din = 1	Q = 000x	Dout = x
350	clock = 1	Din = 1	Q = 1000	Dout = 0
400	clock = 0	Din = 1	Q = 1000	Dout = 0
450	clock = 1	Din = 1	Q = 1100	Dout = 0
500	clock = 0	Din = 1	Q = 1100	Dout = 0
550	clock = 1	Din = 1	Q = 1110	Dout = 0
600	clock = 0	Din = 1	Q = 1110	Dout = 0
650	clock = 1	Din = 1	Q = 1111	Dout = 1
700	clock = 0	Din = 0	Q = 1111	Dout = 1
750	clock = 1	Din = 0	Q = 0111	Dout = 1
800	clock = 0	Din = 0	Q = 0111	Dout = 1
850	clock = 1	Din = 0	Q = 0011	Dout = 1
900	clock = 0	Din = 0	Q = 0011	Dout = 1
950	clock = 1	Din = 0	Q = 0001	Dout = 1


Stopped at time : 1.000 ps : File "C:/Users/gzheng/test/tb.v" Line 29

Graphical Simulation Results

 

Rotate Register

 - Implementation:
 - Connect Q output of one flip flop to the D input of the next flip flop
 - Connect Q output of the last flip flop to the D input of the first flip flop
 - 4-bit rotate register




	OUT(3:0)
Initial value:	0110
rising edge:	0011
rising edge:	1001
rising edge:	1100
rising edge:	0110
rising edge:	0011

Verilog Modeling of Rotate Registers

```
module Barral_Shift_Reg (Q, clock);  
  input clock;  
  output [3:0] Q;  
  
  reg [3:0] Q;  
  
  always @ (posedge clock)  
  begin  
    Q[2:0] <= Q[3:1];  
    Q[3] <= Q[0];  
  end  
  
endmodule
```


Modified Rotate Registers
 
```
module Barral_Shift_Reg (Q, Din, clock, ld);  
  input clock, ld, Din;  
  output [3:0] Q;  
  
  reg [3:0] Q;  
  
  always @ (posedge clock)  
  begin  
    Q[2:0] <= Q[3:1];  
    if (ld) Q[3] <= Din;  
    else   Q[3] <= Q[0];  
  end  
  
endmodule
```




Shift/Rotate Register with Control Input

 - Parallel Load control input may be used to hold the shifting



Universal Shift Register


- Multi-functional shift register

 

- Functions
 - the 4th input of MUX can be used for something else

Inputs		Action
Sh (Shift)	L (Load)	
0	0	no change
0	1	load
1	X	Shift Right



Universal Shift Register

 


Source: www.electronics-tutorials.ws

Shift Register Example: Above-Mirror Display

  
- Earlier example: $8 + 2 + 1 = 11$ wires from computer to registers
- Use shift registers
 - Wires: $1 + 2 + 1 = 4$
 - Computer sends one value at a time, one bit per clock cycle



 Note: this line is 1 bit, rather than 8 bits like before




Application: UART Transmitter

 

Shifters (Not Shift Register)

 - Combinational Datapath component
- Shifting (e.g., left shifting 0011 yields 0110) useful for:
 - Manipulating bits
 - Shift left once is same as multiplying by 2 (0011 (3) becomes 0110 (6))
 - Shift right once same as dividing by 2



Verilog Modeling of Shifter

```
module Shifter_0_or_1 (Q, I, in, sh);
    parameter size = 4;
    input in, sh;
    input [size-1:0] I;
    output [size-1:0] Q;


    reg [size-1:0] Q;

    always @ (sh, in, I)
    begin
        if (sh) begin Q[size-1:1] = I[size-2:0];
                    Q[0]          = in;
                end
        else Q = I;
    end

endmodule
```


Shifter Example: Approximate Celsius to Fahrenheit Converter

 - Convert 8-bit Celsius input to 8-bit Fahrenheit output
 - $F = C * 9/5 + 32$
 - Approximate: $F = C * 2 + 32$
 - Use left shift: $F = \text{left_shift}(C) + 32$




Shifter Example: Temperature Averager

 - Four registers storing a history of temperatures
- Want to output the average of those temperatures
- Add, then divide by four
 - Same as shift right by 2
 - Use three adders, and right shift by two



Bigger Shifter

 - A shifter that can shift by any amount
 - But shifting too many bits in one shifter could require design with too many wires
- More elegant design
 - Chain shifters
 - E.g.: Can achieve any shift of 0..7 bits by enabling the correct combination of 4, 2, 1 bit shifters



Summary

- Register is a storage element
- A flip-flop is a 1-bit register
- How to integrate control signals to register using mux?
- How to control/use registers with control signals?
- Register file is a 2-D memory that uses unique addresses to identify a register/row
- Verilog modeling of registers and register file/2-D memory
- How to load a multi-bit number into a shift register? clocked
- A universal shift register: Parallel-in Serial-out (PISO), PIPO, SIPO, SISO
- Shifter performing multiplication and division, any limitations?